


TEST 2 EE 6140

TEST 2 SOLUTIONS

NAME:

GT ID:

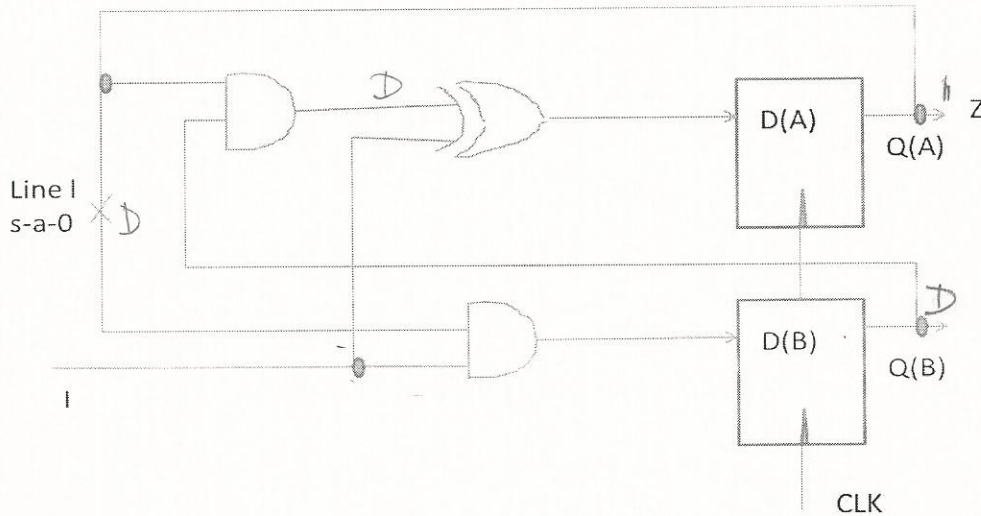Prob 1: For the sequential circuit below and the stuck at zero fault on the line I as shown:



(a) Determine the shortest test sequence assuming the initial states of the flip flops are $Q_1Q_2=00$.

$$I = 1 \quad Q_A^0 Q_B^0 = 00 \quad \text{line } I = 0 \quad \text{starting condition}$$

$$I = 1 \quad Q_A^1 Q_B^1 = 10 \quad \text{line } I = D$$

$$I = 1 \quad Q_A^2 Q_B^2 = 1D \quad \text{line } I = D$$

$$I = 1 \text{ or } 0 \quad Z = \bar{D} \text{ or } D$$


So sequence = 111 or 110

(b) Find if there is a self-initializing test sequence for the fault.

$$D_A = I \oplus (A \cdot B)$$

$$D_B = I \cdot A$$

$$Z = A$$

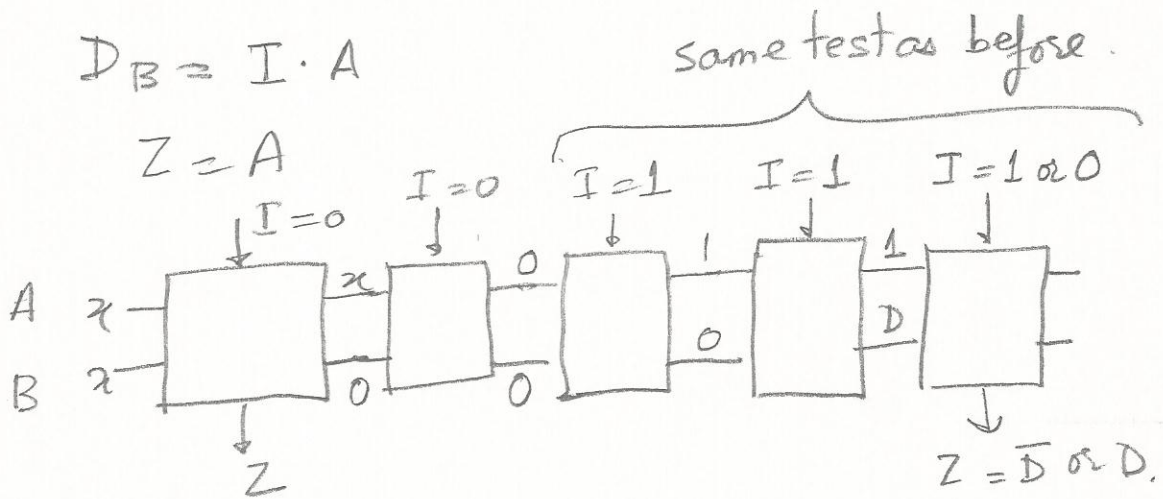


So self-initializing

sequence = 00111

or

00110

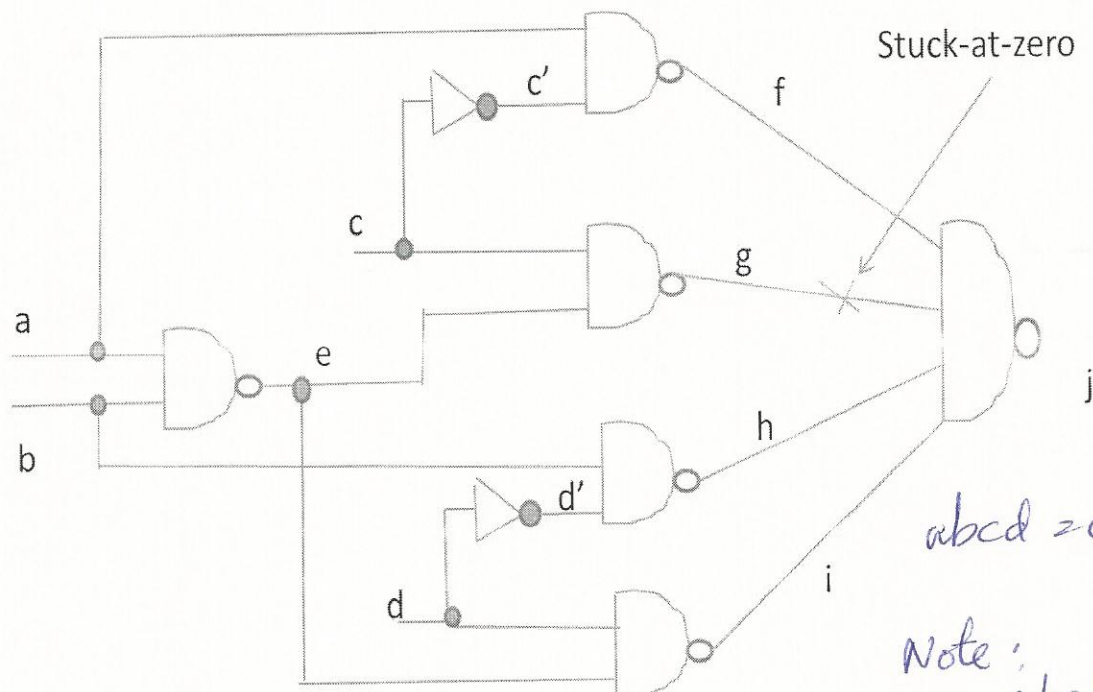Prob 2: Use PODEM to find a test for the line g s-a-0 below.




abcd = 0000 is a test.

Note: abcd = 1111 is also a test

OBJECTIVE	PI ASSIGNMENT	IMPLICATION	D-FRONTIER
$g = 1$	$c = 0$	$c' = 1$	j
$f = 1$	$a = 0$	$f = 1, c' = 1$ $g = D, e = 1$	j
$h = 1$	$b = 0$	$f = 1, c' = 1$ $g = D, e = 1,$ $h = 1$	j
$i = 1$	$d = 0$	$d' = 1, f = 1$ $c' = 1, g = D$ $e = 1, h = 1$ $i = 1, j = D$	<u>SUCCESS</u>

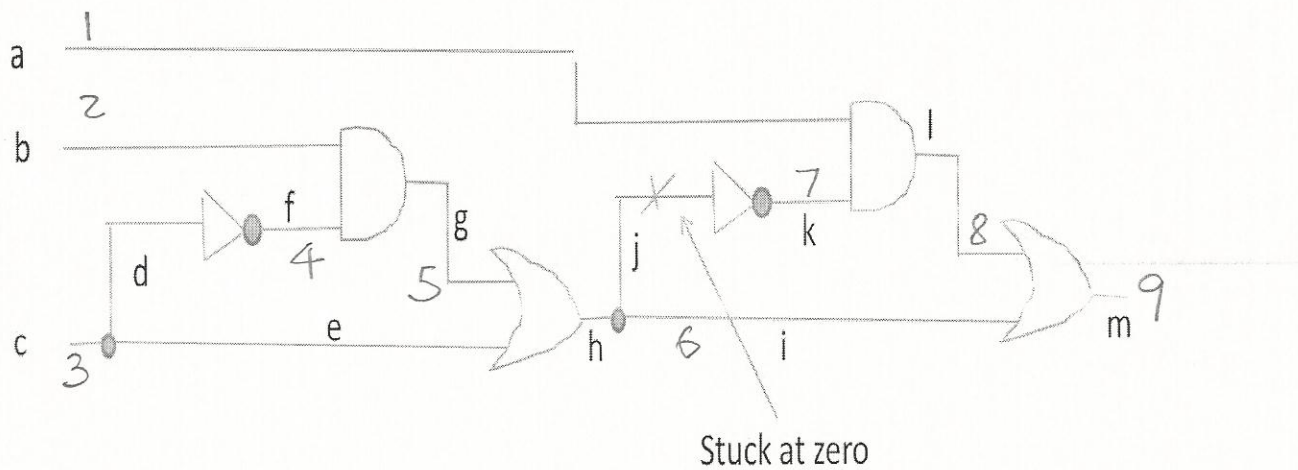Problem 3: For the following circuit show how PODEM handles the fault line j s-a-0.



OBJECTIVE	PI ASSIGNMENT	IMPLICATION	D-FRONTIER
$d = 1$	$c = 1$	$d = 1, f = 0$ $g = 0, m = 1$	x-path check fails.
$d = 1$	$c = 0$	$d = 0, f = 1$	
	$b = 1$	$g = 1, h = 1$	x-path check fails.
	$b = 0$	$h = 0$	test not possible
	$b = x$		
	$c = x$		FAILURE

PROBLEM 4

DECISIONS

IMPLICATIONS

NOTES

Step 1 Excitation

$$g = 1$$

$$g = D$$

$$J-F = \{g\} \quad DF = \{j\}$$

Step 2 D-Drive

$$f = h = i = 1$$

$$d = \overline{D}$$

$$J-F = \{g, f, h, i\}$$

$$DF = \{\text{NULL}\}$$

Step 3 Pick a gate on J-F and set it to controlling value

$$\text{gate} = f$$

$$c' = 0$$

$$c = 1$$

$$\Rightarrow e = 0 \quad (\text{since } g = 1)$$

$$\Rightarrow a = b = 1$$

$$\Rightarrow d' = 0 \quad (\text{since } h = 1)$$

$$\Rightarrow d = 1$$

SUCCESS

so test is $abcd = 1111$

Now see what happens if in step 3 you pick $a = 0$ (worked out in class) - YOU DO THIS AND SEE
