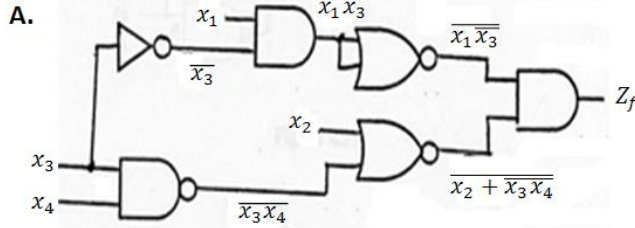




4.3 Determine the output function of the circuit of Figure 4.27 for the following faults:

- AND bridge between inputs of gate G_1
- The multiple fault $\{x_3 s-a-1, x_2 s-a-0\}$




$$Z_f = (x_1x_3)(x_2 + x_3x_4)$$
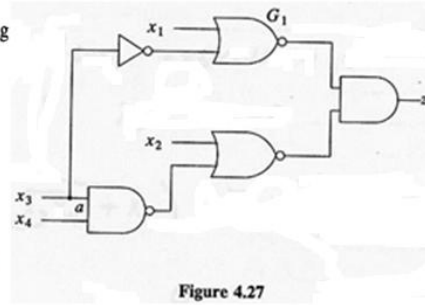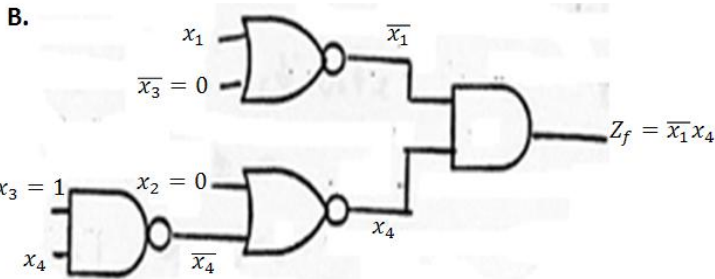
$$= (\overline{x_1} + x_3)(\overline{x_2} \cdot (x_3x_4))$$



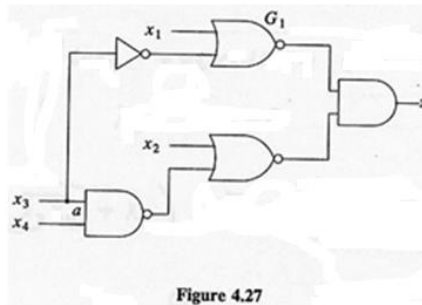4.4 In the circuit of Figure 4.27 which if any of the following tests detect the fault $x_1 s-a-0$?

- (0,1,1,1)
- (1,1,1,1)
- (1,1,0,1)
- (1,0,1,0)



	$Z(t)$	$Z_f(t)$
a. Does not activate	0	0
b. $X_2 = 1 \Rightarrow Z = 0$	0	0
c. $X_2 = 1 \Rightarrow Z = 0$	0	0
d. $X_4 = 0 \Rightarrow Z = 0$	0	0

4.5 For the circuit of Figure 4.27 find a Boolean expression for the set of all tests that detect the fault:

- x_3 s-a-0
- x_2 s-a-0
- x_2 s-a-1

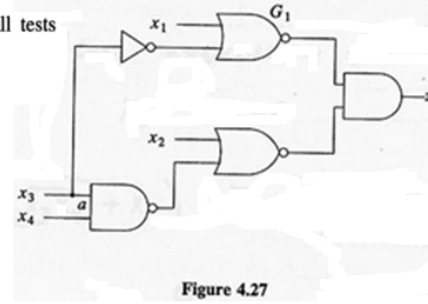


Figure 4.27

A. $Z = (\overline{x_3 x_4} + x_2)(\overline{x_3} + x_1) = \overline{x_1} \overline{x_2} x_3 x_4$
 $Z_f(x_{3s-a-0}) = 0$ (by substitution)

•• set $Z \oplus Z_f = 1$
 $\Rightarrow \overline{x_1} \overline{x_2} x_3 x_4 \oplus 0 = 1$
 $\Rightarrow \overline{x_1} \overline{x_2} x_3 x_4 = 1$
 $\Rightarrow (x_1 x_2 x_3 x_4) = (0011)$ (only **one** test)

B. $Z = \overline{x_1} \overline{x_2} x_3 x_4 \Rightarrow Z_f = \overline{x_1} x_3 x_4$

•• set $Z \oplus Z_f = 1$
 $\Rightarrow \overline{x_1} \overline{x_2} x_3 x_4 \oplus \overline{x_1} x_3 x_4 = 1$
 $\Rightarrow \overline{x_1} x_2 x_3 x_4 = 1$
 $\Rightarrow (x_1 x_2 x_3 x_4) = (0111)$ (only **one** test)

C. $Z = \overline{x_1} \overline{x_2} x_3 x_4$

$Z_f(x_{2s-a-1}) = 0$ (by substitution)

•• set $Z \oplus Z_f = 1$
 $\Rightarrow \overline{x_1} \overline{x_2} x_3 x_4 \oplus 0 = 1$
 $\Rightarrow \overline{x_1} \overline{x_2} x_3 x_4 = 1$
 $\Rightarrow (x_1 x_2 x_3 x_4) = (0011)$ (only **one** test)

4.6 For the circuit of Figure 4.28

- Find the set of all tests that detect the fault c s-a-1.
- Find the set of all tests that detect the fault a s-a-0.
- Find the set of all tests that detect the multiple fault $\{c$ s-a-1, a s-a-0 $\}$.

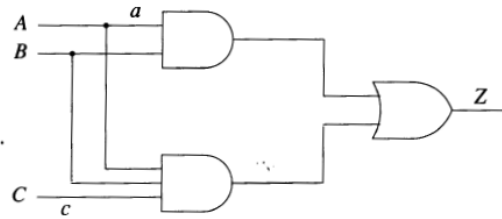


Figure 4.28

A. $Z = AB + ABC = AB$ ($x + xy = x$)

$Z_f = AB + AB(1) = AB$

•• $Z \oplus Z_f = 1$ has no solution

B. $Z = AB + ABC = AB$ (from part A.)

$Z_f = (0)B + ABC = ABC$

•• $Z \oplus Z_f = 1 \Rightarrow AB \oplus ABC = 1$
 $\Rightarrow A = 1, B = 1, C = 0$

C. $Z = AB + ABC = AB$ (from part A.)

$Z_f = (0)B + AB(1) = 0 + AB = AB$

•• $Z \oplus Z_f = 1 \Rightarrow AB \oplus AB = 1$
 \Rightarrow which has no solution

4.8 For the circuit of Figure 4.30

- Find the set of all tests that detect the fault $b \text{ s-a-1}$.
- Find the set of all tests that distinguish the faults $a \text{ s-a-0}$ and $c \text{ s-a-0}$.
- Find the set of all tests that distinguish the multiple faults $\{a \text{ s-a-0}, b \text{ s-a-1}\}$ and $\{c \text{ s-a-0}, b \text{ s-a-1}\}$.

A. $Z_1 = \bar{C} + AB$

$$Z_2 = AB + ABC = AB$$

$$Z_{1f(b \text{ s-a-1})} = \bar{C} + AB \quad (\text{same as } Z_1)$$

$$Z_{2f(b \text{ s-a-1})} = AB + AB(1) = AB \quad (\text{same as } Z_2)$$

●● $b \text{ s-a-1}$ is not detectable

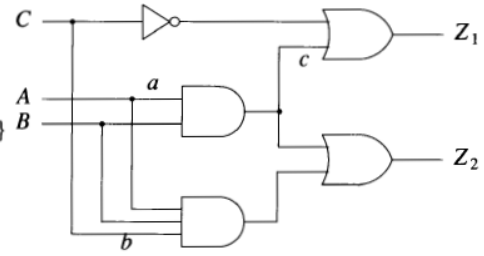


Figure 4.30

B. For $a \text{ s-a-0}$: $Z_{1f} = \bar{C}$ and $Z_{2f} = ABC$

For $c \text{ s-a-0}$: $Z_{1f} = \bar{C}$ and $Z_{2f} = AB + ABC = AB$

●● $Z_f \oplus Z_g = 1 \Rightarrow Z_{1f} \oplus Z_{1g} = \bar{C} \oplus \bar{C} = 1$ no solution

$\Rightarrow Z_{2f} \oplus Z_{2g} = AB \oplus ABC = 1 \Rightarrow AB\bar{C} = 1 \Rightarrow ABC = 110$

C. ●● $m_1 = \{a \text{ s-a-0}, b \text{ s-a-1}\}$ ●● $m_2 = \{c \text{ s-a-0}, b \text{ s-a-1}\}$

Under m_1 : $Z_{1m_1} = \bar{C}$, $Z_{2m_1} = AB$

Under m_2 : $Z_{1m_2} = \bar{C}$, $Z_{2m_2} = AB + AB = AB$

Therefore m_1 and m_2 are indistinguishable