

PRACTICE FINAL SOLUTIONS

FINAL EXAM: ECE 6140 FALL 2011

NAME:

GT ID NO:

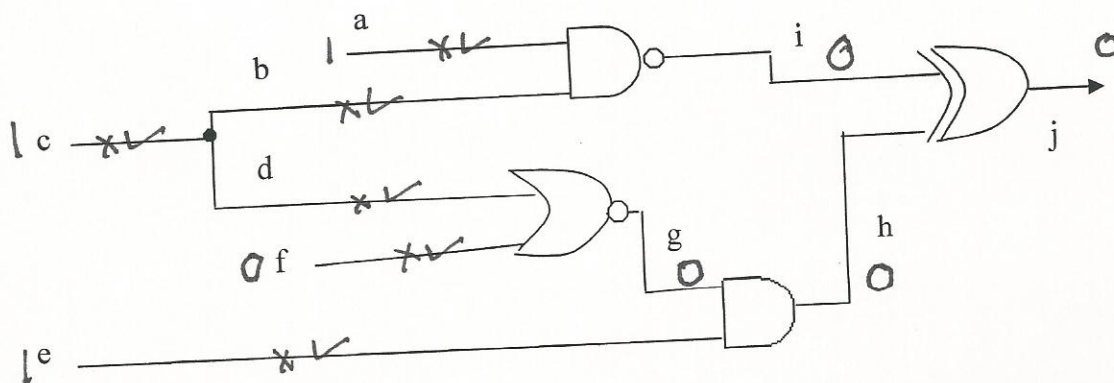


Figure 1. Test Ckt.

Prob 1 (10 points): For the fault set $\{a_0, a_1, b_0, b_1, c_0, c_1, d_0, d_1, e_0, e_1, f_0, f_1\}$ in Figure 1, perform deductive fault simulation with the input vector $acfe = [1, 1, 0, 1]$. Give all the fault lists below.

$$L_a = \{a_0\}$$

$$L_b = \{c_0, b_0\}$$

$$L_c = \{c_0\}$$

$$L_d = \{c_0, d_0\}$$

$$L_e = \{e_0\}$$

$$L_f = \{f_1\}$$

$$L_g = L_d - L_f = \{c_0, d_0\}$$

$$L_h = L_g - L_e = \{c_0, d_0\}$$

$$L_i = L_a \cup L_b = \{a_0, b_0, c_0\}$$

$$L_j = (L_h \cup L_i) - (L_h \cap L_i) = \{a_0, b_0, d_0\}$$

The following faults are detected = a_0, b_0, d_0

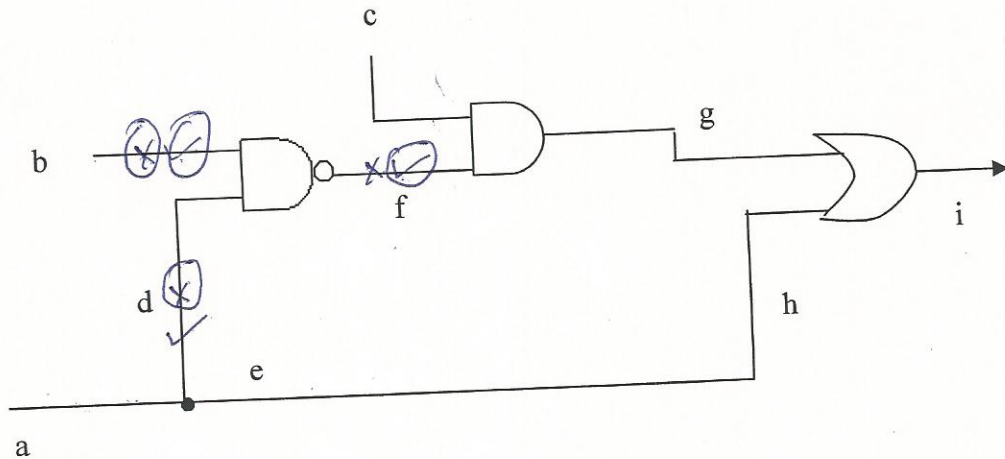


Figure 2. Test Ckt.

Prob 2 (10 points): For the circuit of Figure 2, identify *all* the redundant faults in the circuit if any or say that all faults are detectable.

$$F = (\overline{a \cdot b}) \cdot c + a$$

$$= \overline{a} \cdot c + \overline{b} \cdot c + a = a + c + \overline{b} \cdot c$$

$$= a + c(1 + \overline{b})$$

$$= a + c$$

$$\{b_0, b_1, f_1, d_0\}$$

Prob 3 (10 points): For the circuit of Figure 3:

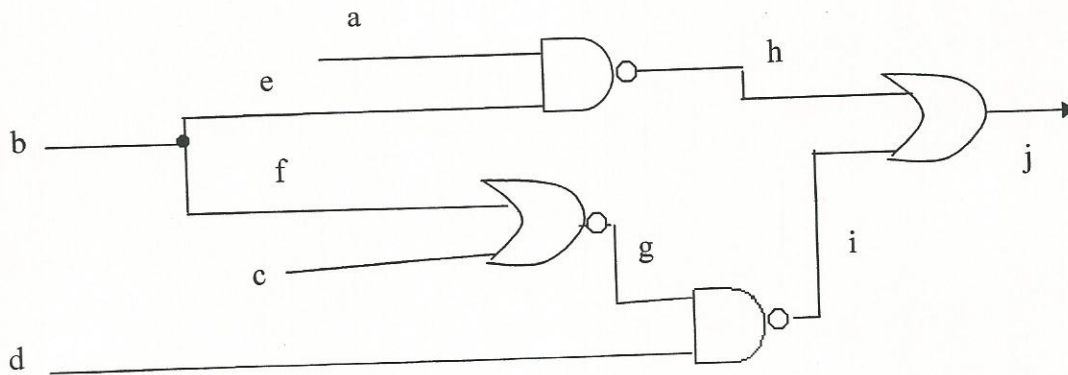


Figure 3. Test Ckt.

There are 20 stuck-at faults in the circuit of Figure 3, 2 in each of the lines a thru j. Starting with all 20 faults, reduce the fault set using equivalent and dominant fault collapsing as follows (*read carefully*).

Using crosses (stuck at 0) and ticks (stuck at 1), show the set of faults in the Figure below *after only equivalent fault collapsing*:

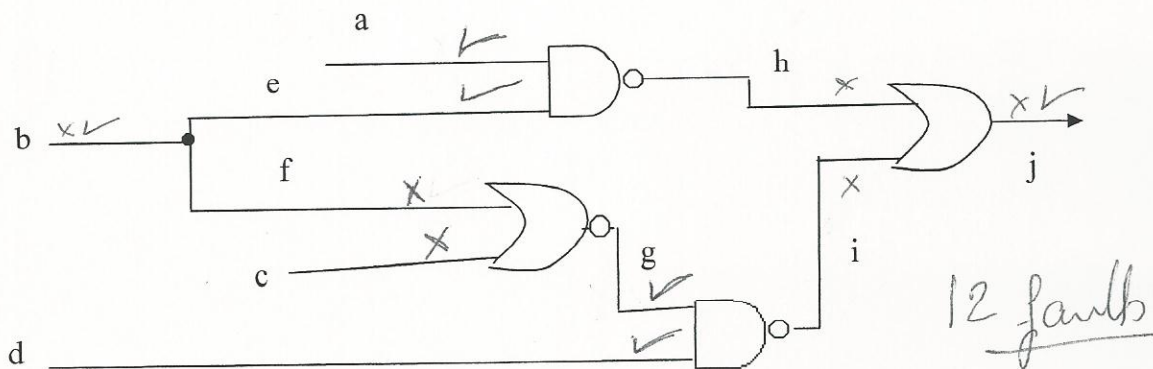


Figure 3a. Test Ckt after Equivalent fault collapsing

Now, using crosses (stuck at 0) and ticks (stuck at 1) again, show the set of faults remaining after performing equivalent *and* dominant fault collapsing in Figure 3b (i.e. perform dominant fault collapsing on the faults remaining in Figure 3a).



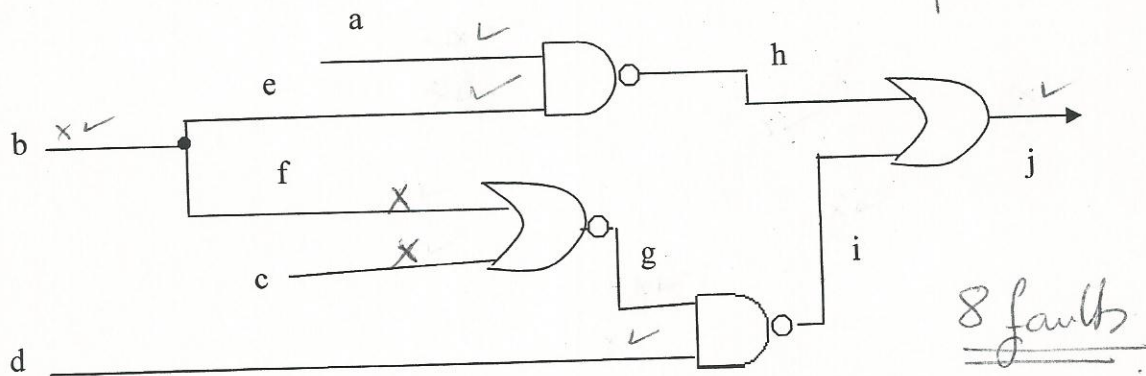


Figure 3b. Test Ckt after Equivalent *and* Dominant fault collapsing

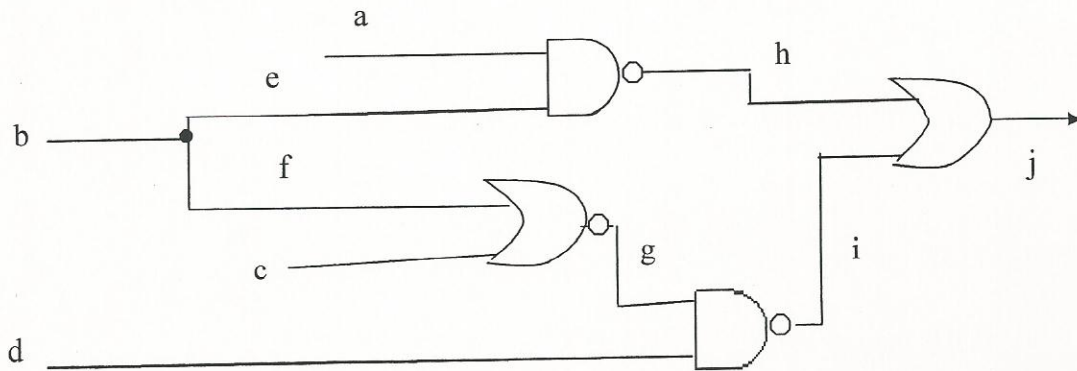You may use the figures below for rough work:



Rough Work:

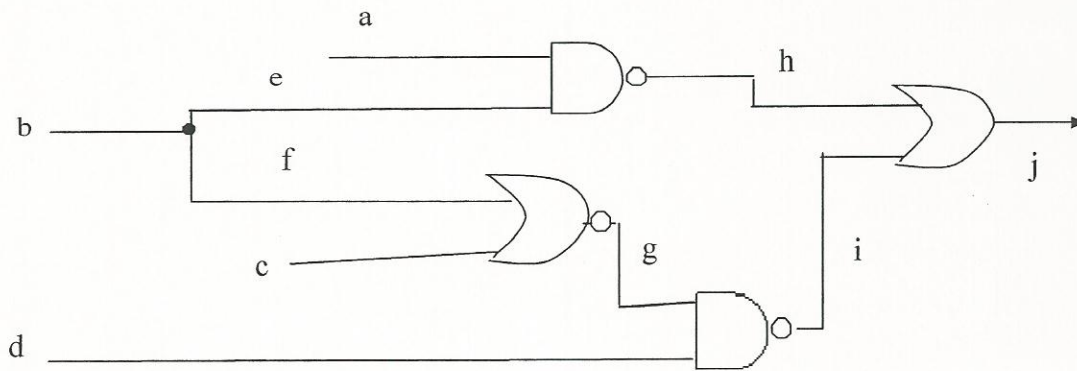

Rough Work:

$$\begin{aligned}
 g_f &= a \cdot d + \overline{(b+c)} \cdot a \cdot d \\
 &= a \cdot d + b + c + \bar{a} + \bar{d} \\
 &= d + \bar{a} + \bar{d} + b + c = 1
 \end{aligned}$$

$$\begin{aligned}
 g &= a + \overline{(b+c)} \cdot d \\
 &= a + \overline{b \cdot c} + \bar{d} = a + b + c + \bar{d}
 \end{aligned}$$

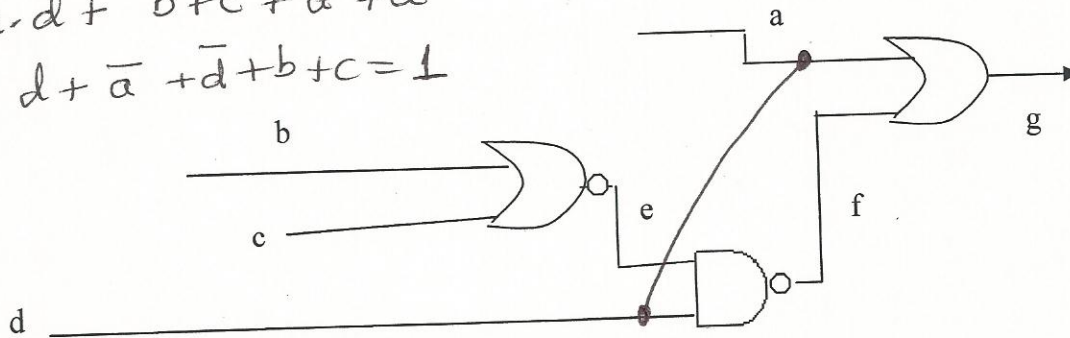


Figure 4. Test Circuit.

Prob 4 (10 points): Give a list of *ALL* the test vectors that detect the AND type bridging fault between lines d and a in Figure 4.

Tests abcd = 0001

So vector is $1 \oplus (a+b+c+\bar{d}) = 1$

or abcd = 0001

Give a list of vectors that distinguish between the above bridging fault and the fault line e stuck-at-1.

Tests abcd =

$$1 \oplus (\bar{d} + a) = 1$$

$$f_{\text{bridge}} = 1$$

$$f_{e=1} = \bar{d} + a$$

$$a=0, d=1$$

$$abcd = \begin{bmatrix} 0001 \\ 0011 \\ 0101 \\ 0111 \end{bmatrix}$$


PROB 5 (10 points): Consider an LFSR for which $P^*(x) = x^3 + x + 1$.

(a) What is the signature (remainder) for a data sequence for which $G(x) = x^6 + x^4 + x + 1$.

$R(x) =$

$$\begin{array}{r}
 x^3 + 1 \\
 x^3 + x + 1 \overline{) x^6 + x^4 + x + 1} \\
 \underline{x^6 + x^4 + x^3} \\
 x^3 + x + 1 \\
 \underline{x^3 + x + 1} \\
 0
 \end{array}$$

(b) Draw the LFSR below.

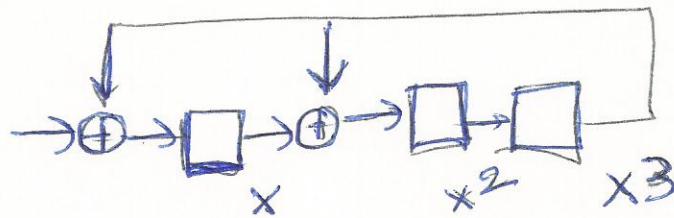

(c) Give one erroneous data sequence (erroneous generator polynomial for data sequence) that will give the same signature as the data sequence in part (a) above.

$$\text{signature} = \text{Rem of } G(x)/P^*(x) = S$$

$$\text{under error } G'(x) = G(x) + E(x)$$

$$\text{so signature under error } S^* = \text{Rem of } \left(\frac{G(x) + E(x)}{P^*(x)} \right)$$

By the Chinese Remainder Theorem

$$S^* = \text{Rem} \left(\frac{G(x)}{P^*(x)} \right) + \text{Rem} \left(\frac{E(x)}{P^*(x)} \right)$$

Aliasing occurs when $S^* = S$. This happens when

$$\text{Rem} \left(\frac{E(x)}{P^*(x)} \right) = 0 \quad \text{or } E(x) = \text{multiple of } P^*(x)$$

$$\text{So pick any } E(x) = (1 + d_1x + d_2x^2 + \dots) P^*(x)$$

$$d_i = \{0, 1\}$$

Pick $d_1 = 1$, all other $d_i = 0$

$$E(x) = (1+x)(x^3+x+1) = x^4 + x^3 + x^2 + 1$$

$$G'(x) = G(x) + E(x) = x^6 + \cancel{x^4} + x + 1 + \cancel{x^4} + x^3 + x^2 + 1$$

$$= x^6 + x^3 + x^2 + x = \text{ANSWER.}$$

$$\text{Check that } \text{Rem} \left(\frac{x^6 + x^4 + x + 1}{x^3 + x + 1} \right) = \text{Rem} \left(\frac{x^6 + x^3 + x^2 + x}{x^3 + x + 1} \right)$$

Note: you could have picked

$$E(x) = (x+x^2)(x^3+x+1) \text{ as well}$$

$$(\text{try it and find } q'(x) = q(x) + E(x))$$

PROB 6 (10 points) A FSM has two flip flops with outputs A and B and inputs D(A) and D(B) respectively. The FSM has an input I and one output Z. The equations for the FSM are given below (XOR = Exclusive-OR).

$$D(A) = A \text{ OR } B$$

$$D(B) = A \text{ XOR } I$$

$$Z = B$$

(XOR = exclusive OR, OR = logical OR)

Initially, at $t=0$, $A(0) = B(0) = 0$.

Starting with the above initial states, find a test sequence of *minimal* length that detects the fault D(A) stuck-at-0.

So any $E(x) = (1 + d_1x + d_2x^2 + \dots) p^*(x)$ where $x = \{0, 1\}$ will give same remainder as

PROB 6 (10 points) A FSM has two flip flops with outputs A and B and inputs D(A) and D(B) respectively. The FSM has an input I and one output Z. The equations for the FSM are given below (XOR = Exclusive-OR).

$$D(A) = A \text{ OR } B$$

$$D(B) = A \text{ XOR } I$$

$$Z = B$$

(XOR = exclusive OR, OR = logical OR)

Initially, at $t=0$, $A(0) = B(0) = 0$.

Starting with the above initial states, find a test sequence of *minimal* length that detects the fault D(A) stuck-at-0.

