

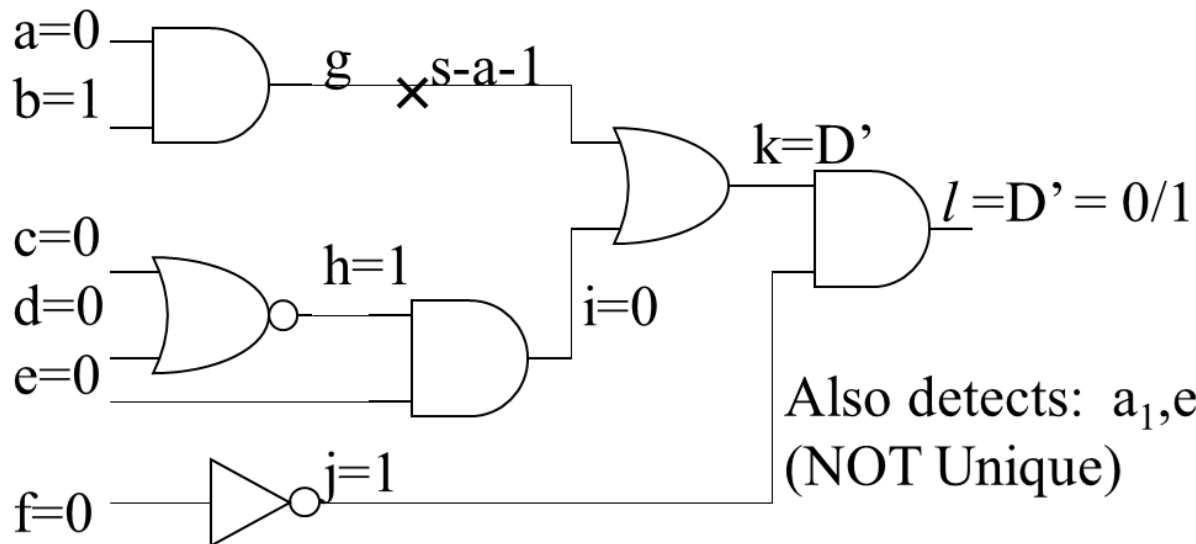


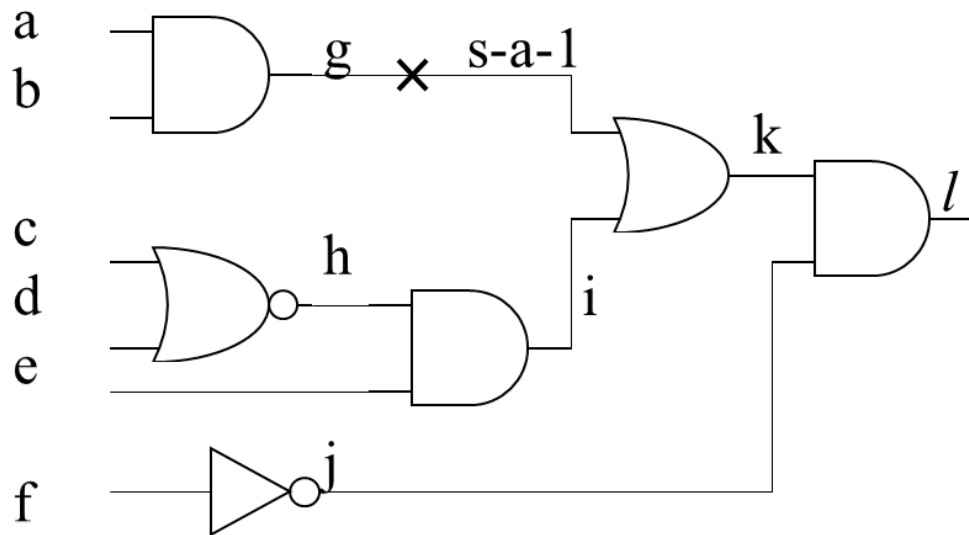6.1 – Generate a test for g s-a-1. List all other faults detected.



Also detects: a_1, e_1, i_1, k_1, l_1
(NOT Unique)

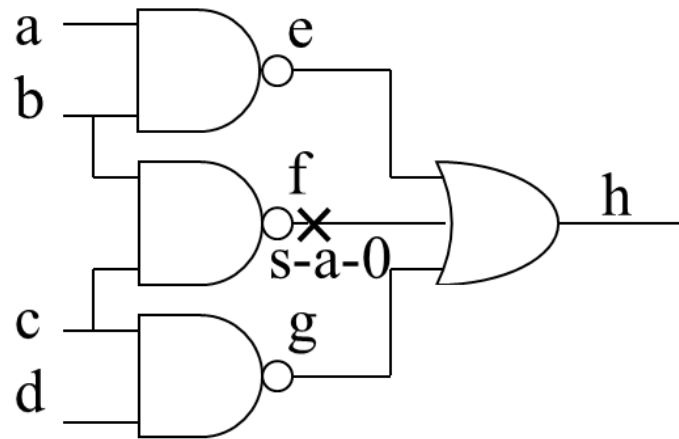6.3 – Use only implications to show that the fault f s-a-0 is undetectable.



SOLUTION:

f s-a-0 requires $f=1$ (activation)

Unique D-drive thru h implies $e=0$, and $g=0$

$e=0$ implies $a=b=1$

$g=0$ implies $c=d=1$

$b=1$ and $c=1$ implies $f=0$ (CONTRADICTION)

6.4 – Construct a 5-value truth table for a 2-input XOR gate.


XOR	0	1	D	D'	x
0	0	1	D	D'	X
1	1	0	D'	D	X
D	D	D'	0	1	X
D'	D'	D	1	0	X
X	X	X	X	X	X

6.5 – Can a gate on the D-frontier have both D and D' among its input values?


SOLUTION:

YES. However, it will not propagate to the gate output.

For example:

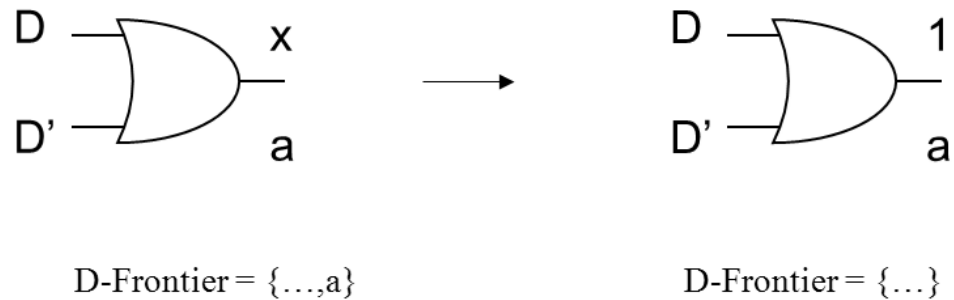

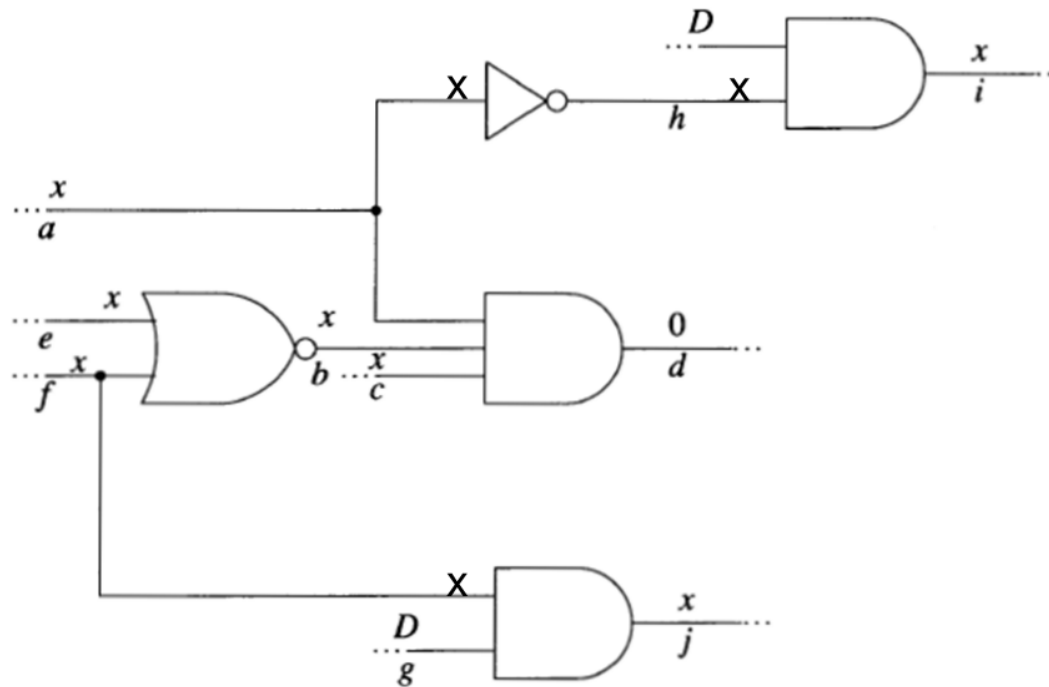
6.8 – Assume that trying to justify $d=0$ via $a=0$ failed as a result of an inconsistency. Reverse the decision and perform all implications.



Objective	Assignment	Action	Implication
$d=0$	$a=0$	conflict, backtrack	$d=0, h=1$
$d=0$	$a=1, c=0$	objective is met	$h=0, i=0$


← i.e. pick another input

6.12 – Apply PODEM to:

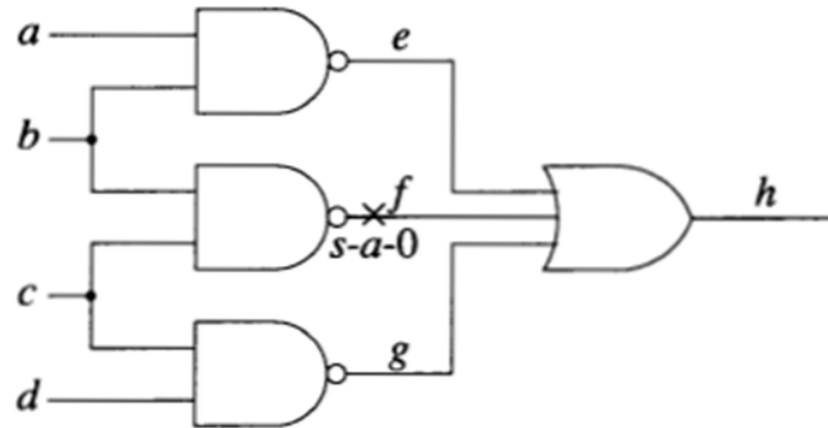


Decision Tree



objective	$f=1$
backtrace to PI	Set $b=0$
imply	Failure ($e=1 \Rightarrow h=1$) X
reverse decision	Set $b=1$
backtrace to PI	Set $c=0$
imply	Failure ($g=1 \Rightarrow h=1$) X
reverse decision	Set $c=1$
imply	Failure $f=0$ X

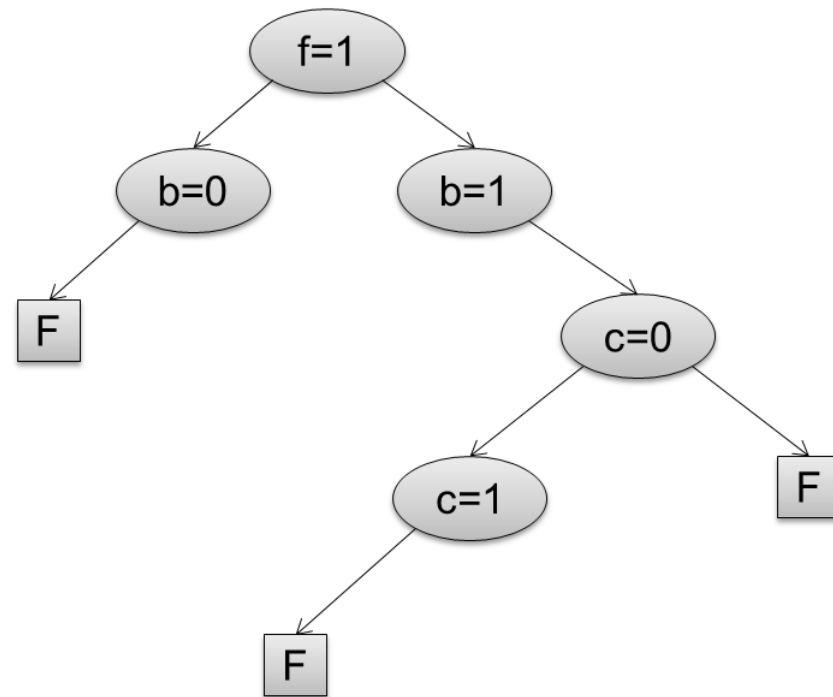

6.12 – Apply PODEM to:

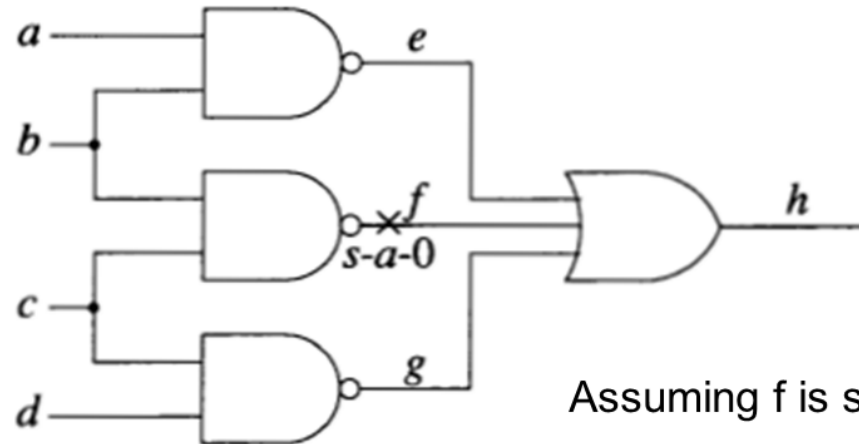

Assuming f is set

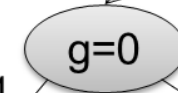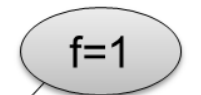


c=1

c=0




Decision Tree

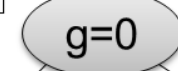


d=1

d=0

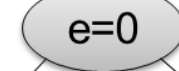

a=1

a=0

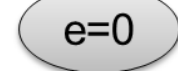

b=1

b=0



objective f=1

objective g=0

assign c=1

assign d=1


objective e=0

assign a=1

assign b=1 ➡ Failure (b,c=1,1 ➡ f=0) X

•• Backtrack ➡ b=0 ➡ Failure (i.e. ➡ e=1) X

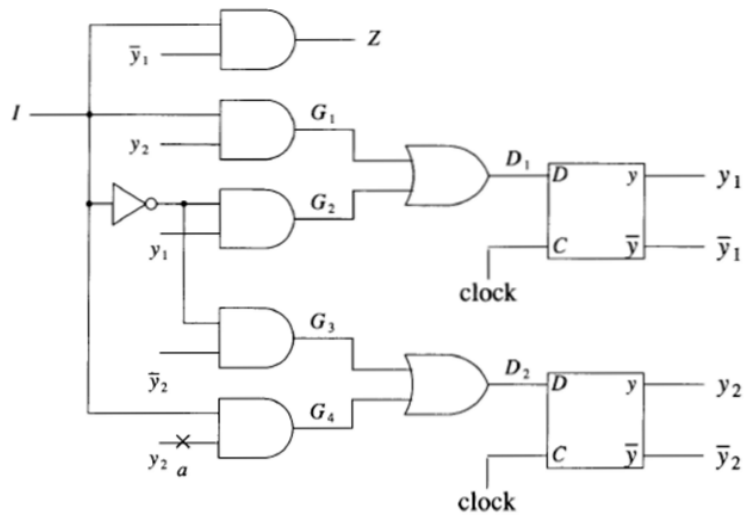
6.32 – Derive a test sequence for Z s-a-0.



(a)

(a) Assume an initial state of ($q_1=q_2=1$)

	I	q_1	q_2	q_1^+	q_2^+	Z
Timeframe 1	0	1	1	1	0	0
Timeframe 2	1	1	0	0	0	0
Timeframe 3	1	0	0			1

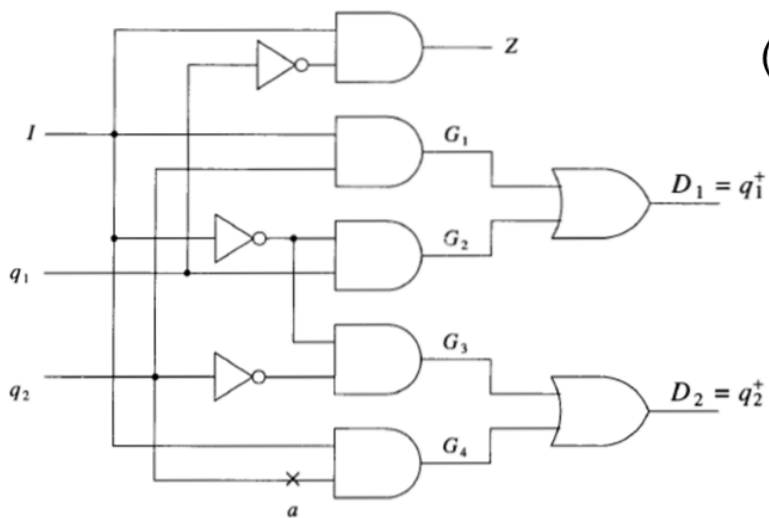

(b)

(b) Assume an unknown initial state (x, x)

If $I=0$ then next states are (x, x)

If $I=1$ then next states are (x, x)

Can not initialize!!