 


Characteristics of Fault Simulation

- ❑ Fault activity with respect to fault-free circuit
 - is often **sparse** both in **time** and **space**.
- ❑ For example
 - F1 is not activated by the given pattern, while F2 affects only the lower part of this circuit.



57

Fault Simulation Techniques

- ❑ Parallel Fault Simulation
- ❑ Deductive Fault Simulation

58



Parallel Fault Simulation

- ❑ Simulate multiple circuits simultaneously
 - The inherent parallel operation of computer words to simulate faulty circuits in parallel with fault-free circuit
 - The number of faulty circuits or faults can be processed simultaneously is limited by the word length, e.g., 32 circuits for a 32-bit computer
- ❑ Complication
 - An event or a value change of a single faulty or fault-free circuit leads to the computation of an entire word
 - The fault-free logic simulation is repeated for each pass

59

Parallel Fault Simulation

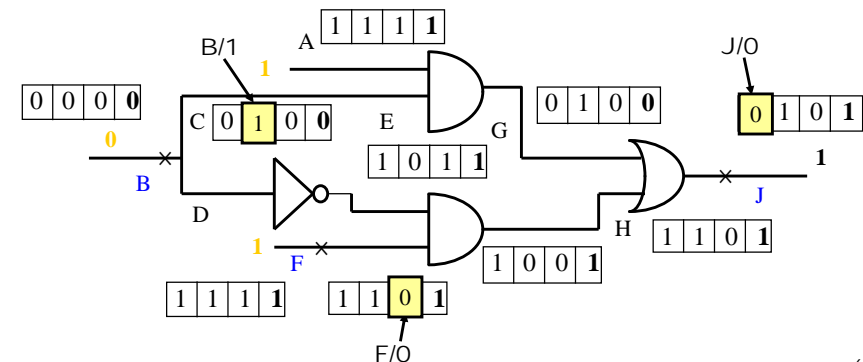 - ❑ Example
 - Consider three faults: (J s-a-0, B s-a-1, and F s-a-0)
 - Bit-space: (FF denotes fault-free)



60


Deductive Fault Simulation

- Simulate all faulty circuits in one pass
 - For each pattern, sweep the circuit from PIs to POs.
 - During the process, a **list of faults** is associated with each wire
 - The list contains faults that would produce a **fault effect** on this wire
 - The **union fault list** at every PO contains the detected faults by the simulated input vector
- Main operation is **fault list propagation**
 - Depending on gate types and values
 - The size of the list may grow dynamically, leading to the potential memory explosion problem

61

Illustration of Fault List Propagation

Consider a two-input AND-gate:

 

Non-controlling case:

Case 1: $A=1, B=1, C=1$ at fault-free,
 $LC = LA \cup LB \cup \{C/0\}$

Controlling cases:

Case 2: $A=1, B=0, C=0$ at fault-free,
 $LC = (\overline{LA} \cap LB) \cup \{C/1\}$

Case 3: $A=0, B=0, C=0$ at fault-free,
 $LC = (LA \cap LB) \cup \{C/1\}$

\overline{LA} is the set of all faults not in LA

62

Rule of Fault List Propagation


	<i>a</i>	<i>b</i>	<i>z</i>	Output fault list
AND	0	0	0	$\{L_a \cap L_b\} \cup Z_1$
	0	1	0	$\{L_a - L_b\} \cup Z_1$
	1	0	0	$\{L_b - L_a\} \cup Z_1$
	1	1	1	$\{L_a \cup L_b\} \cup Z_0$
OR	0	0	0	$\{L_a \cup L_b\} \cup Z_1$
	0	1	1	$\{L_b - L_a\} \cup Z_0$
	1	0	1	$\{L_a - L_b\} \cup Z_0$
	1	1	1	$\{L_a \cap L_b\} \cup Z_0$
NOT	0		1	$L_a \cup Z_0$
	1		0	$L_a \cup Z_1$

63

Deductive Fault Simulation

□ Example (1/4)

 - Consider 3 faults: $B/1$, $F/0$, and $J/0$ under $(A,B,F) = (1,0,1)$



Fault list at PIs:


$LB = \{B/1\}$, $LF = \{F/0\}$, $LA = \emptyset$, $LC=LD = \{B/1\}$

64

Deductive Fault Simulation

 Example (2/4)

- Consider 3 faults: B/1, F/0, and J/0 under $(A,B,F) = (1,0,1)$



$LB = \{B/1\}$, $LF = \{F/0\}$, $LA = \emptyset$, $LC = LD = \{B/1\}$

Fault lists at G and E:

$LG = (LA \cap LC) \cup G/1 = \{B/1, G/1\}$


$LE = (LD) \cup E/0 = \{B/1, E/0\}$

65

Deductive Fault Simulation

 Example (3/4)

- Consider 3 faults: B/1, F/0, and J/0 under $(A,B,F) = (1,0,1)$



$LB = \{B/1\}$, $LF = \{F/0\}$, $LA = \emptyset$, $LC = LD = \{B/1\}$,

$LG = \{B/1, G/1\}$, $LE = \{B/1, E/0\}$

Fault list at H:


$LH = (LE \cup LF) \cup LH = \{B/1, E/0, F/0, H/0\}$

66

Deductive Fault Simulation

 Example (4/4)

- Consider 3 faults: B/1, F/0, and J/0 under $(A,B,F) = (1,0,1)$



$LB = \{B/1\}$, $LF = \{F/0\}$, $LA = \emptyset$, $LC = LD = \{B/1\}$, $LG = \{B/1, G/1\}$, $LE = \{B/1, E/0\}$, $LH = \{B/1, E/0, F/0, H/0\}$

Final fault list at PO J:


$LJ = (LH - LG) \cup LJ = \{E/0, F/0, J/0\}$

67

Deductive Fault Simulation

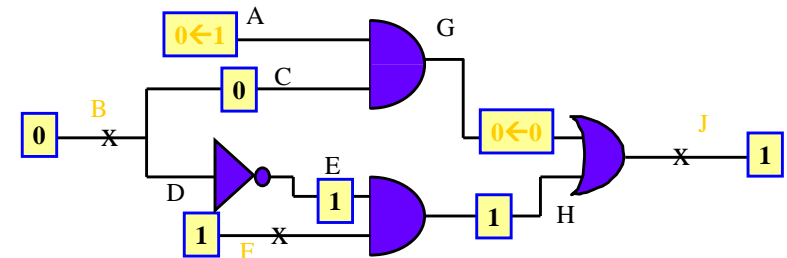Example (cont'd)

- Consider 3 faults: B/1, F/0, and J/0 under $(A,B,F) = (0,0,1)$



Event driven updates:

$LB = \{B/1\}$, $LF = \{F/0\}$, $LA = \emptyset$, $LC = LD = LE = \{B/1\}$,

$LG = \{G/1\}$, $LH = \{B/1, F/0\}$, $LJ = \{B/1, F/0, J/0\}$

68


Outline

- Fault Modeling
- Fault Simulation
- Automatic Test Pattern Generation (ATPG)
 - Functional approach
 - Boolean difference
 - Structural approach
 - D-algorithm
 - PODEM
- Design for Testability

69

Typical ATPG Flow

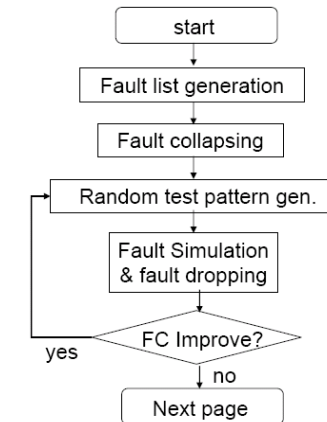
- 1st phase: random test pattern generation



70

Typical ATPG Flow (cont'd)

 - 2nd phase: deterministic test pattern generation



71

Test Pattern Generation

- The test set T of a fault α with respect to some PO z can be computed by

$$T(x) = z(x) \oplus z_{\alpha}(x)$$

- A test pattern can be fully specified or partially specified depending on whether the values of PIs are all assigned
 - Example


abc	z	z_{α}
000	0	0
001	0	0
010	0	0
011	0	0
100	0	0
101	1	1
110	1	0
111	1	0

Input vectors (1,1,0) and (1,1,-) are fully and partially specified test patterns of fault α , respectively.

72

Structural Test Generation D-Algorithm

- Test generation from circuit structure
- Two basic goals
 - (1) Fault activation (FA)
 - (2) Fault propagation (FP)
 - Both of which requires Line Justification (LJ), i.e., finding input combinations that force certain signals to their desired values
- Notations:
 - 1/0 is denoted as D, meaning that good-value is 1 while faulty value is 0
 - Similarly, 0/1 is denoted as D'
 - Both D and D' are called fault effects (FE)

 


73

Structural Test Generation D-Algorithm


- Fault activation
 - Setting the faulty signal to either 0 or 1 is a Line Justification problem
- Fault propagation
 - (1) select a path to a PO → decisions
 - (2) Once the path is selected → a set of line justification (LJ) problems are to be solved
- Line justification
 - Involves decisions or implications
 - Incorrect decisions: need backtracking

 To justify $c=1 \rightarrow a=1$ and $b=1$ (implication)
To justify $c=0 \rightarrow a=0$ or $b=0$ (decision)



74

 Structural Test Generation D-Algorithm: Fault Propagation




- Fault activation
 - $G1=0 \rightarrow \{a=1, b=1, c=1\} \rightarrow \{G3=0\}$
- Fault propagation: through G5 or G6
- Decision through G5:
 - $G2=1 \rightarrow \{d=0, a=0\} \rightarrow$ inconsistency at a → backtrack !!
- Decision through G6:
 - $\rightarrow G4=1 \rightarrow e=0 \rightarrow$ done !! The resulting test is (111x0)

D-frontiers: are the gates whose output value is x, while one or more inputs are D or D'. For example, initially, the D-frontier is { G5, G6 }.

75

 Structural Test Generation D-Algorithm: Line Justification



- FA → set h to 0
- FP → $e=1, f=1 (\rightarrow o=0)$; FP → $q=1, r=1$
- To justify $q=1 \rightarrow l=1$ or $k=1$
- Decision: $l=1 \rightarrow c=1, d=1 \rightarrow m=0, n=0 \rightarrow r=0 \rightarrow$ inconsistency at r → backtrack !
- Decision: $k=1 \rightarrow a=1, b=1$
- To justify $r=1 \rightarrow m=1$ or $n=1 (\rightarrow c=0$ or $d=0) \rightarrow$ Done ! (J-frontier is ϕ)

J-frontier: is the set of gates whose output value is known (i.e., 0 or 1), but is not implied by its input values.
Ex: initially, J-frontier is {q=1, r=1}

76

Test Generation

- A branch-and-bound search
- Every decision point is a **branching** point
- If a set of decisions lead to a **conflict**, a **backtrack** is taken to explore other decisions
- A **test is found** when
 - (1) fault effect is propagated to a PO, and
 - (2) all internal lines are justified
- No test is found after all possible decisions are tried → Then, target fault is **undetectable**
- Since the search is **exhaustive**, it will find a test if one exists

For a combinational circuit, an **undetectable** fault is also a **redundant** fault
→ Can be used to simplify circuit.


77

Implication

- Implication
 - Compute the values that can be uniquely determined
 - **Local implication**: propagation of values from one line to its immediate successors or predecessors
 - **Global implication**: the propagation involving a larger area of the circuit and re-convergent fanout
- Maximum implication principle
 - Perform as many implications as possible
 - It helps to either reduce the number of problems that need decisions or to **reach an inconsistency sooner**


78

Forward Implication

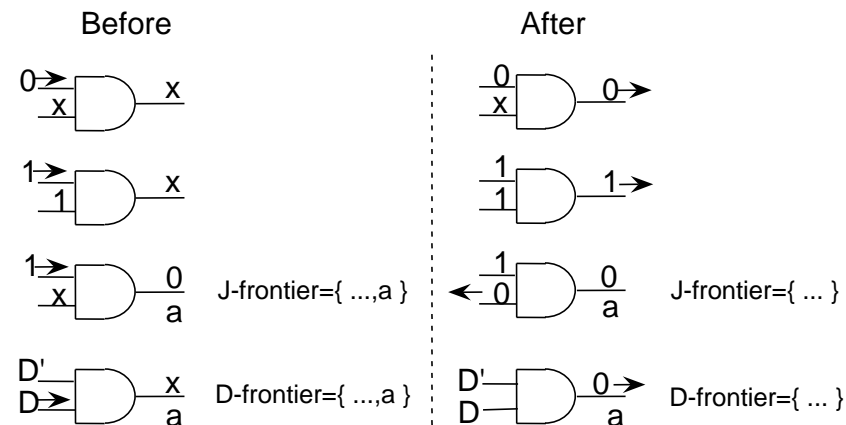

79

Backward Implication

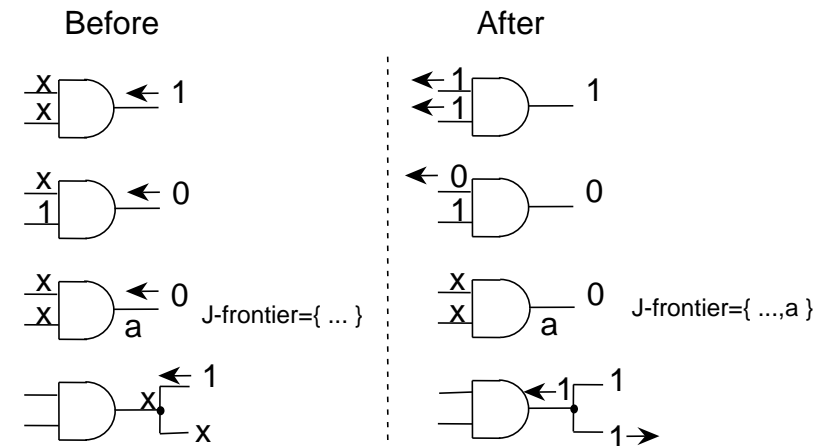


80

D-Algorithm (1/4)

Example

- Five logic values {0, 1, x, D, D'}

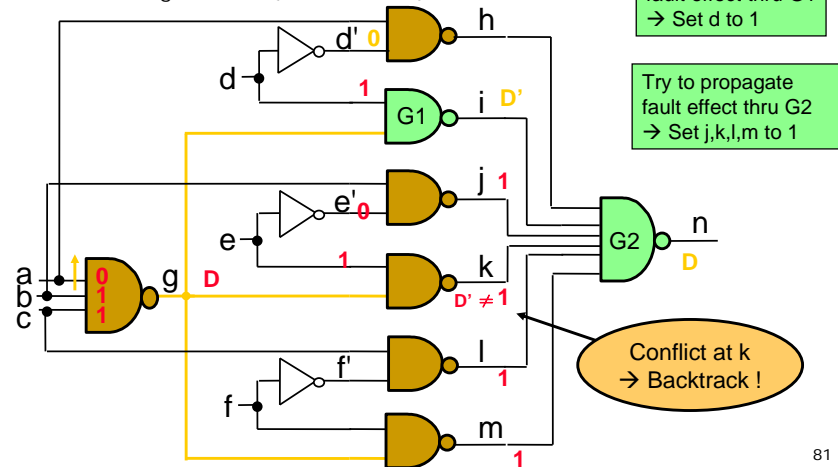


81

D-Algorithm (2/4)

Example

- Five logic values {0, 1, x, D, D'}

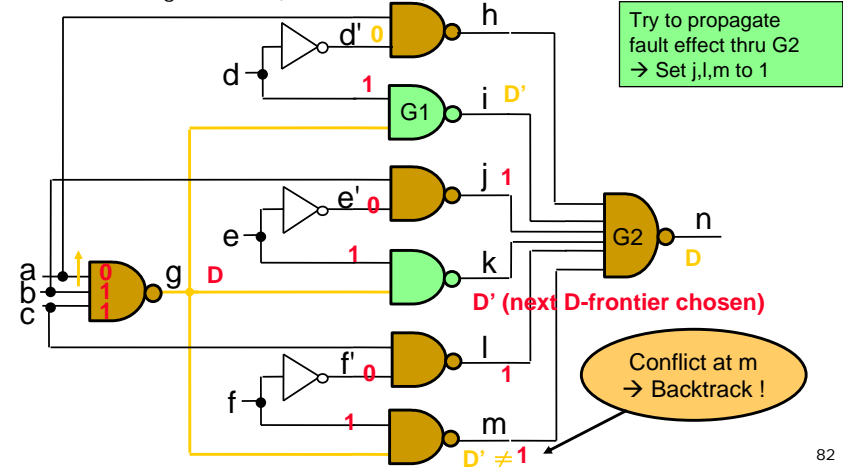


82

D-Algorithm (3/4)

Example

- Five logic values {0, 1, x, D, D'}

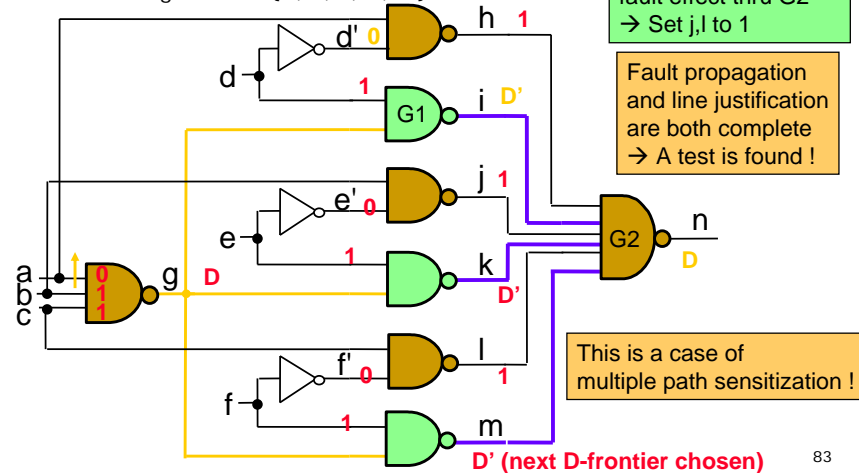

83

D-Algorithm (4/4)


Decision	Implication	Comments
	a=0 h=1 b=1 c=1 g=D	Active the fault Unique D-drive
d=1	i=D' d'=0	Propagate via i
j=1 k=1 l=1 m=1	n=D e'=0 e=1 k=D'	Propagate via n Contradiction

e=1	k=D' e'=0 j=1	Propagate via k
l=1 m=1	n=D f'=0 f=1 m=D'	Propagate via n Contradiction
f=1	m=D' f'=0 l=1 n=D	Propagate via m

84

Decision Tree on D-Frontier

 - The decision tree
 - Node → D-frontier
 - Branch → decision taken
 - A **Depth-First-Search** (DFS) strategy is often used



85


PODEM Algorithm

- PODEM: **Path-Oriented DEcision Making**
- Fault Activation (FA) and Propagation (FP)
 - lead to sets of Line Justification (LJ) problems. The LJ problems can be solved via value assignments.
- In D-algorithm
 - TG is done through **indirect signal assignment** for FA, FP, and LJ, that eventually maps into **assignments at PI's**
 - The **decision points** are at **internal lines**
 - The worst-case number of **backtracks is exponential** in terms of the number of decision points (e.g., at least 2^k for k decision nodes)
- In PODEM
 - The test generation is done through a sequence of **direct assignments at PI's**
 - Decision points are at PIs, thus the number of **backtracking** might be **fewer**

86

PODEM Algorithm Search Space of PODEM

 - Complete search space
 - A binary tree with 2^n leaf nodes, where n is the number of PIs
- Fast test generation
 - Need to find a path leading to a SUCCESS terminal quickly



87

PODEM Algorithm Objective and Backtrace

- PODEM
 - Also aims at establishing a sensitization path based on **fault activation and propagation** like D-algorithm
 - Instead of justifying the signal values required for sensitizing the selected path, objectives are setup to guide the **decision process at PIs**
- Objective
 - is a **signal-value pair** (w, v_w)
- Backtrace
 - Backtrace **maps a desired objective into a PI assignment** that is likely to contribute to the achievement of the objective
 - Is a process that traverses the circuit back from the objective signal to PIs
 - The result is a **PI signal-value pair** (x, v_x)
 - **No signal value is actually assigned during backtrace (toward PI) !**

88

PODEM Algorithm Objective

Objective routine involves

- selection of a **D-frontier**, G
- selection of an **unspecified input gate** of G

```

Objective() {
  /* The target fault is w s-a-v */
  /* Let variable obj be a signal-value pair */
  if (the value of w is x) obj = ( w, v' );
  else {
    select a gate (G) from the D-frontier;
    select an input (j) of G with value x;
    c = controlling value of G;
    obj = (j, c');
  }
  return (obj);
}
    
```

← fault activation

← fault propagation

89

PODEM Algorithm Backtrace

Backtrace routine involves

- finding an all-x path from objective site to a PI, i.e., every signal in this path has value x


```

Backtrace(w, v_w) {
  /* Maps objective into a PI assignment */
  G = w; /* objective node */
  v = v_w; /* objective value */
  while (G is a gate output) { /* not reached PI yet */
    inv = inversion of G;
    select an input (j) of G with value x;
    G = j; /* new objective node */
    v = v ⊕ inv; /* new objective value */
  }
  /* G is a PI */ return (G, v);
}
    
```

90

PODEM Algorithm PI Assignment

 PIs: { a, b, c, d }
 Current Assignments: { a=0 }
 Decision: b=0 → objective fails
 Reverse decision: b=1
 Decision: c=0 → objective fails
 Reverse decision: c=1
 Decision: d=0



Failure means fault effect cannot be propagated to any PO under current PI assignments

91

PODEM Algorithm

PODEM () /* using depth-first-search */

begin

```


If(error at PO) return(SUCCESS);
If(test not possible) return(FAILURE);
(k, v_k) = Objective(); /* choose a line to be justified */
(j, v_j) = Backtrace(k, v_k); /* choose the PI to be assigned */
Imply (j, v_j); /* make a decision */
If ( PODEM() == SUCCESS ) return (SUCCESS);
Imply (j, v_j'); /* reverse decision */
If ( PODEM() == SUCCESS ) return(SUCCESS);
Imply (j, x);
Return (FAILURE);
    
```

end

92

PODEM Algorithm (1/4)


Example

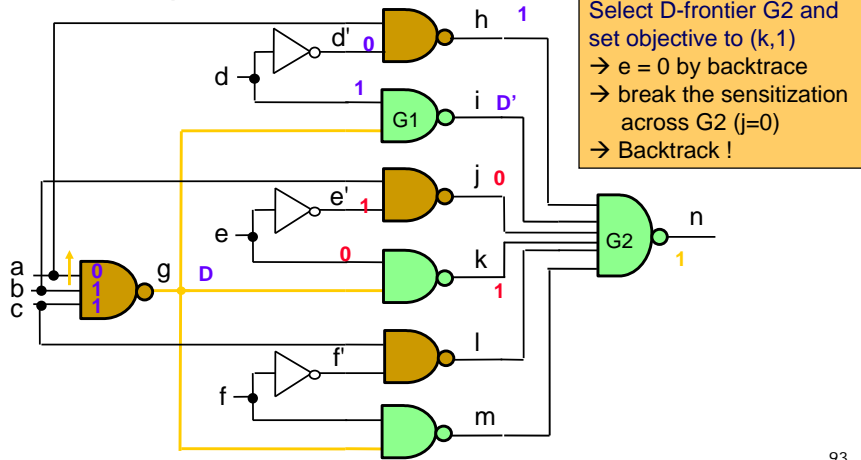

93

PODEM Algorithm (2/4)


Example

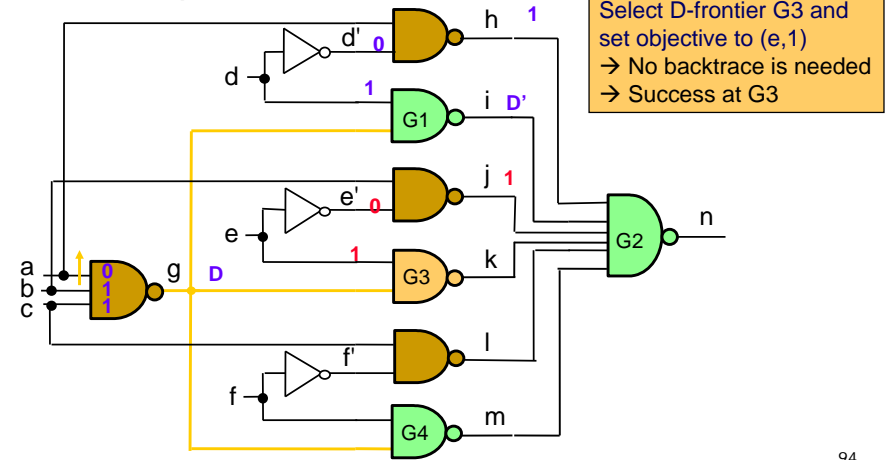

94

PODEM Algorithm (3/4)


Example

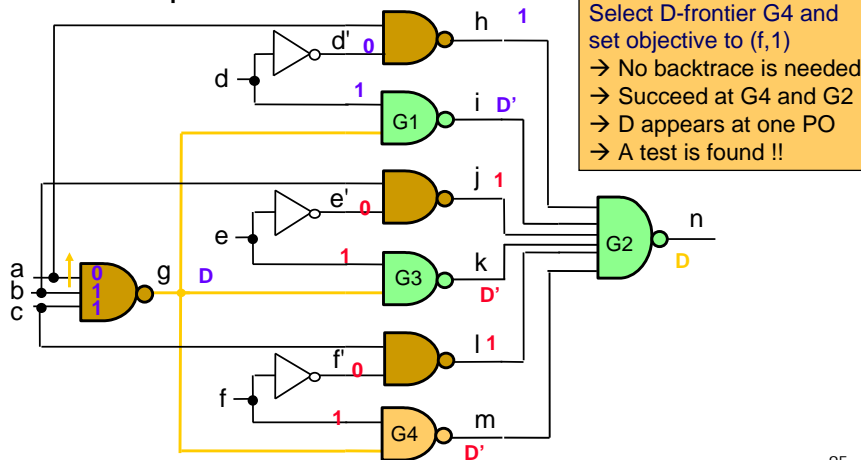

95

PODEM Algorithm (4/4)


Objective	PI assignment	Implications	D-frontier	Comments
a=0	a=0	h=1	g	
b=1	b=1		g	
c=1	c=1	g=D	i,k,m	
d=1	d=1	d'=0		
		i=D'	k,m,n	
k=1	e=0	e'=1 j=0 k=1 n=1		Assignments need to be reversed during backtracking
	e=1	e'=0 j=1 k=D'	m	no solutions! → backtrack flip PI assignment
l=1	f=1	f'=0 l=1 m=D' n=D	m,n	

 

96

PODEM Algorithm Decision Tree

 - Decision node:
PI selected through backtrace for value assignment
- Branch:
value assignment to the selected PI



97

Termination Conditions

- D-algorithm
 - Success:
 - (1) Fault effect at an output (D-frontier may not be empty)
 - (2) J-frontier is empty
 - Failure:
 - (1) D-frontier is empty (all possible paths are false)
 - (2) J-frontier is not empty
- PODEM
 - Success:
 - Fault effect seen at an output
 - Failure:
 - Every PI assignment leads to failure, in which D-frontier is empty while fault has been activated

98

PODEM Overview

- PODEM
 - examines all possible input patterns implicitly but exhaustively (branch-and-bound) for finding a test
 - complete like D-algorithm (i.e., will find a test if exists)
- Other key features
 - No J-frontier, since there are no values that require justification
 - No consistency check, as conflicts can never occur
 - No backward implication, because values are propagated only forward
 - Backtracking is implicitly done by simulation rather than by an explicit and time-consuming save/restore process
 - Experiments show that PODEM is generally faster than D-algorithm

99

Outline

- Fault Modeling
- Fault Simulation
- Automatic Test Pattern Generation
- Design for Testability

100

Why DFT ?

- Direct testing is way too difficult !
 - Large number of FFs
 - Embedded memory blocks
 - Embedded analog blocks

101

Design for Testability

- Definition
 - Design for testability (DFT) refers to those design techniques that make test generation and testing cost-effective
- DFT methods
 - Ad-hoc methods, full and partial scan, built-in self-test (BIST), boundary scan
- Cost of DFT
 - Pin count, area, performance, design-time, test-time, etc.

102


Important Factors

- Controllability
 - Measure the ease of controlling a line
- Observability
 - Measure the ease of observing a line at PO
- DFT deals with ways of improving
 - Controllability and observability

103


Test Point Insertion

 - Employ test points to enhance **controllability** and **observability**
 - CP: Control Points
 - Primary inputs used to enhance controllability
 - OP: Observability Points
 - Primary outputs used to enhance observability



104

Control Point Insertion

 

- Normal operation:
When CP_enable = 0
- Inject 0:
Set CP_enable = 1 and CP = 0
- Inject 1:
Set CP_enable = 1 and CP = 1

105

Control Point Selection

□ Goal

- Controllability of the fanout-cone of the added point is improved

□ Common selections

- Control, address, and data buses
- Enable/hold inputs
- Enable and read/write inputs to memory
- Clock and preset/clear signals of flip-flops
- Data select inputs to multiplexers and demultiplexers

106

Observation Point Selection

□ Goal

- Observability of the transitive fanins of the added point is improved

□ Common choice


- Stem lines with more fanouts
- Global feedback paths
- Redundant signal lines
- Output of logic devices having many inputs
 - MUX, XOR trees
- Output from state devices
- Address, control and data buses

107

 Problems with Test Point Insertion

□ Large number of I/O pins

- Can be resolved by adding MUXs to reduce the number of I/O pins, or by adding shift-registers to impose CP values



108

What Is Scan ?

Objective

- To provide controllability and observability at **internal state variables** for testing

Method


- Add **test mode** control signal(s) to circuit
- Connect **flip-flops to form shift registers** in test mode
- Make inputs/outputs of the flip-flops in the shift register controllable and observable

Types

- Internal scan
 - Full scan, partial scan, random access
- Boundary scan


109

Scan Concept

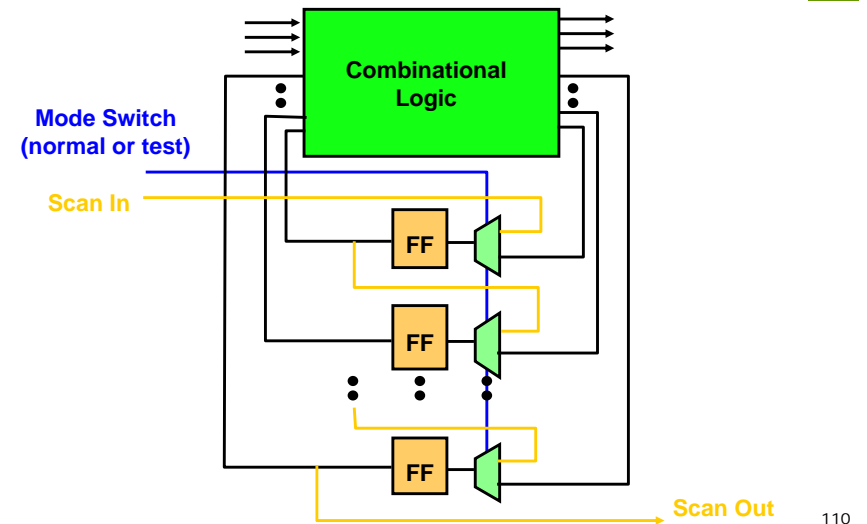

110


Logic Design before Scan Insertion

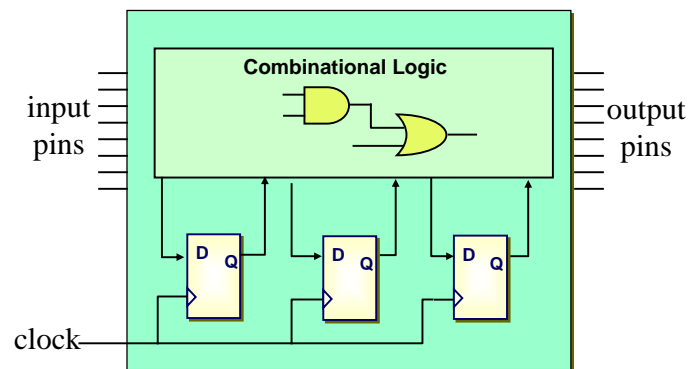

Sequential ATPG is extremely difficult:
due to the lack of controllability and observability at flip-flops.

111

Logic Design after Scan Insertion

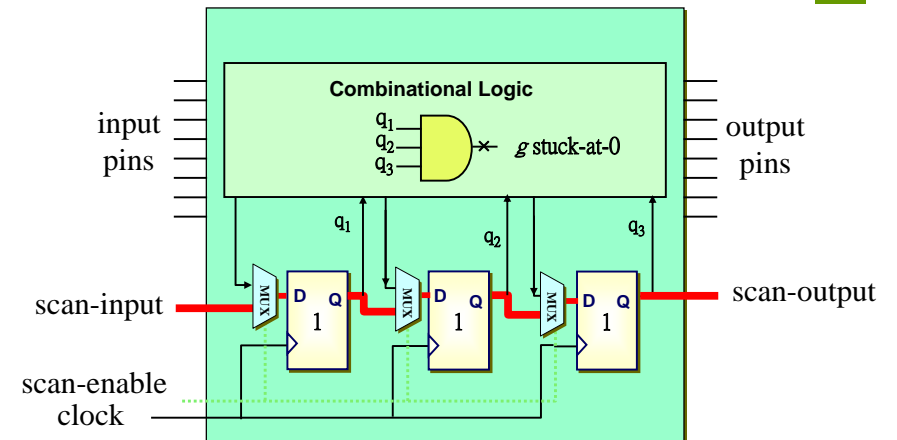


Scan Chain provides an easy access to flip-flops
→ Pattern generation is much easier !!

112

Scan Insertion

- Example
 - 3-stage counter

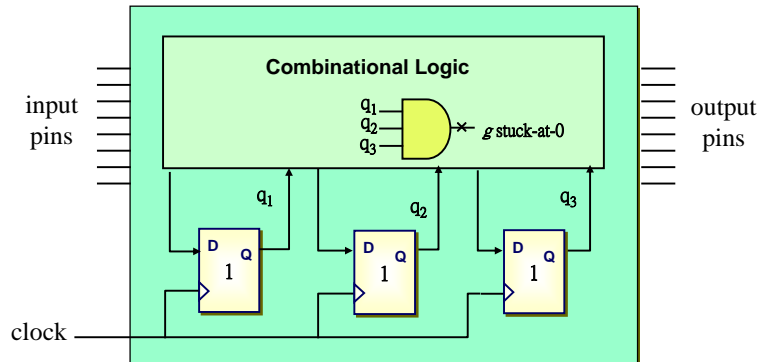

It takes 8 clock cycles to set the flip-flops to be (1, 1, 1), for detecting the target fault g stuck-at-0 fault (2^{20} cycles for a 20-stage counter !)

113

Overhead of Scan Design

- Case study
 - #CMOS gates = 2000
 - Fraction of flip-flops = 0.478
 - Fraction of normal routing = 0.471

Scan implementation	Predicted overhead	Actual area overhead	Normalized operating frequency
None	0	0	1.0
Hierarchical	14.05%	16.93%	0.87
Optimized	14.05%	11.9%	0.91

114


Full Scan Problems

- Problems
 - Area overhead
 - Possible performance degradation
 - High test application time
 - Power dissipation
- Features of commercial tools
 - Scan-rule violation check (e.g., DFT rule check)
 - Scan insertion (convert a FF to its scan version)
 - ATPG (both combinational and sequential)
 - Scan chain reordering after layout

115

Scan-Chain Reordering

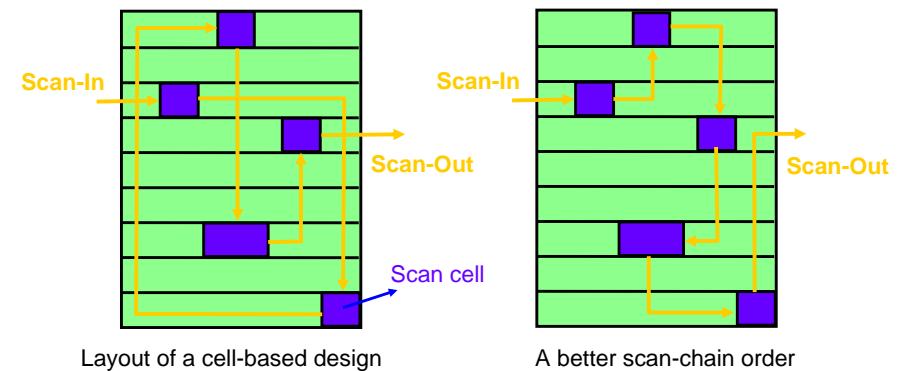- Scan-chain order is often decided at gate-level *without knowing the cell placement*
- Scan-chain consumes a lot of *routing resources*, and could be minimized by *re-ordering the flip-flops* in the chain after layout is done



116

Partial Scan

□ Basic idea

- Select a **subset of flip-flops** for scan
- Lower overhead (area and speed)
- Relaxed design rules

□ Cycle-breaking technique


- **Cheng & Agrawal**, IEEE Trans. On Computers, April 1990
- Select scan flip-flops to **simplify sequential ATPG**
- Overhead is about **25% off** than full scan

□ Timing-driven partial scan

- **Jou & Cheng**, ICCAD, Nov. 1991
- Allow optimization of area, timing, and testability simultaneously

117


Full Scan vs. Partial Scan

 

scan time	longer	shorter
hardware overhead	more	less
fault coverage	~100%	unpredictable
ease-of-use	easier	harder

118

Area Overhead vs. Test Effort

 

119

Conclusions

□ Testing

- Conducted after manufacturing
- Must be considered during the design process

□ Major fault models

- Stuck-at, bridging, stuck-open, delay fault, ...

□ Major tools needed

- Design-for-Testability
 - By scan chain insertion or built-in self-test
- Fault simulation
- ATPG

□ Other Applications in CAD

- ATPG is a way of Boolean reasoning and is applicable to many logic-domain CAD problems

120