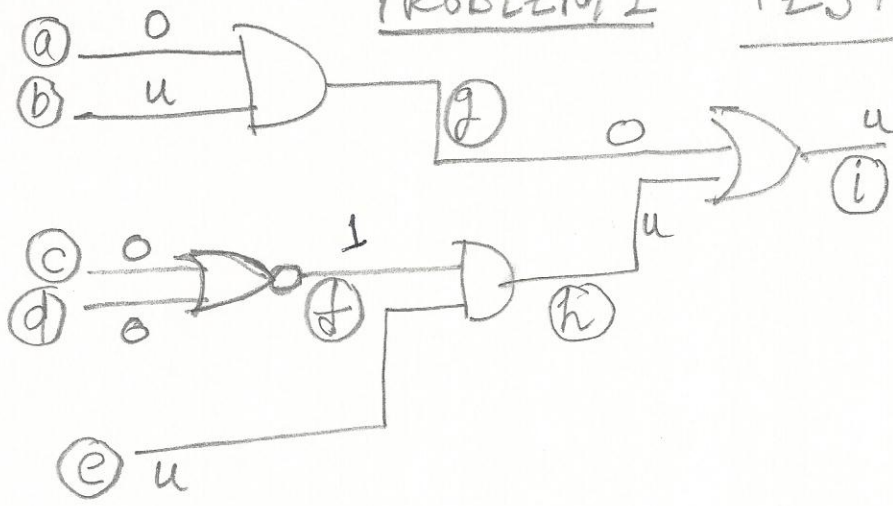


PROBLEM 1 TEST 1 SOLUTIONS



$$L_a^1 = \{a_1\}$$

$$L_a^u = \{\emptyset\}$$

$$L_b^1 = \{b_1\}$$

$$L_b^0 = \{b_0\}$$

$$L_c^1 = \{c_1\}$$

$$L_c^u = \{\emptyset\}$$

$$L_d^1 = \{d_1\}$$

$$L_d^u = \{\emptyset\}$$

$$L_e^1 = \{e_1\}$$

$$L_e^0 = \{e_0\}$$

$$L_f^0 = L_c^1 \cup L_d^1 = \{c_1, d_1\}$$

$$\begin{aligned} L_f^u &= \overline{L_c^1} \cap \overline{L_d^1} - (\overline{L_c^1 \cup L_c^u}) \cap (\overline{L_d^1 \cup L_d^u}) \\ &= \overline{\{c_1\}} \cap \overline{\{d_1\}} - \overline{\{c_1\}} \cap \overline{\{d_1\}} \\ &= \{\emptyset\} \end{aligned}$$

$$L_g^1 = L_a^1 \cap L_b^1 = \{\emptyset\}$$

$$\begin{aligned} L_g^u &= (L_a^1 \cup L_a^u) \cap \overline{L_b^0} \\ &\quad - (L_a^1 \cap L_b^1) \\ &= \{a_1\} \end{aligned}$$

$$L_h^1 = \overline{L_f^0} \cap L_f^u \cap L_e^1 = \{e_1\}$$


$$L_h^0 = L_f^0 \cup L_e^0 = \{c_1, d_1, e_0\}$$

$$L_i^1 = L_g^1 \cup L_h^1 = \{e_1\}$$

$$\begin{aligned} L_i^0 &= \overline{(L_g^u \cup L_g^1)} \cap L_h^0 \\ &= \overline{\{a_1\}} \cap \{c_1, d_1, e_0\} \end{aligned}$$


$$= \{c_1, d_1, e_0\}$$

TEST PROBLEM 2

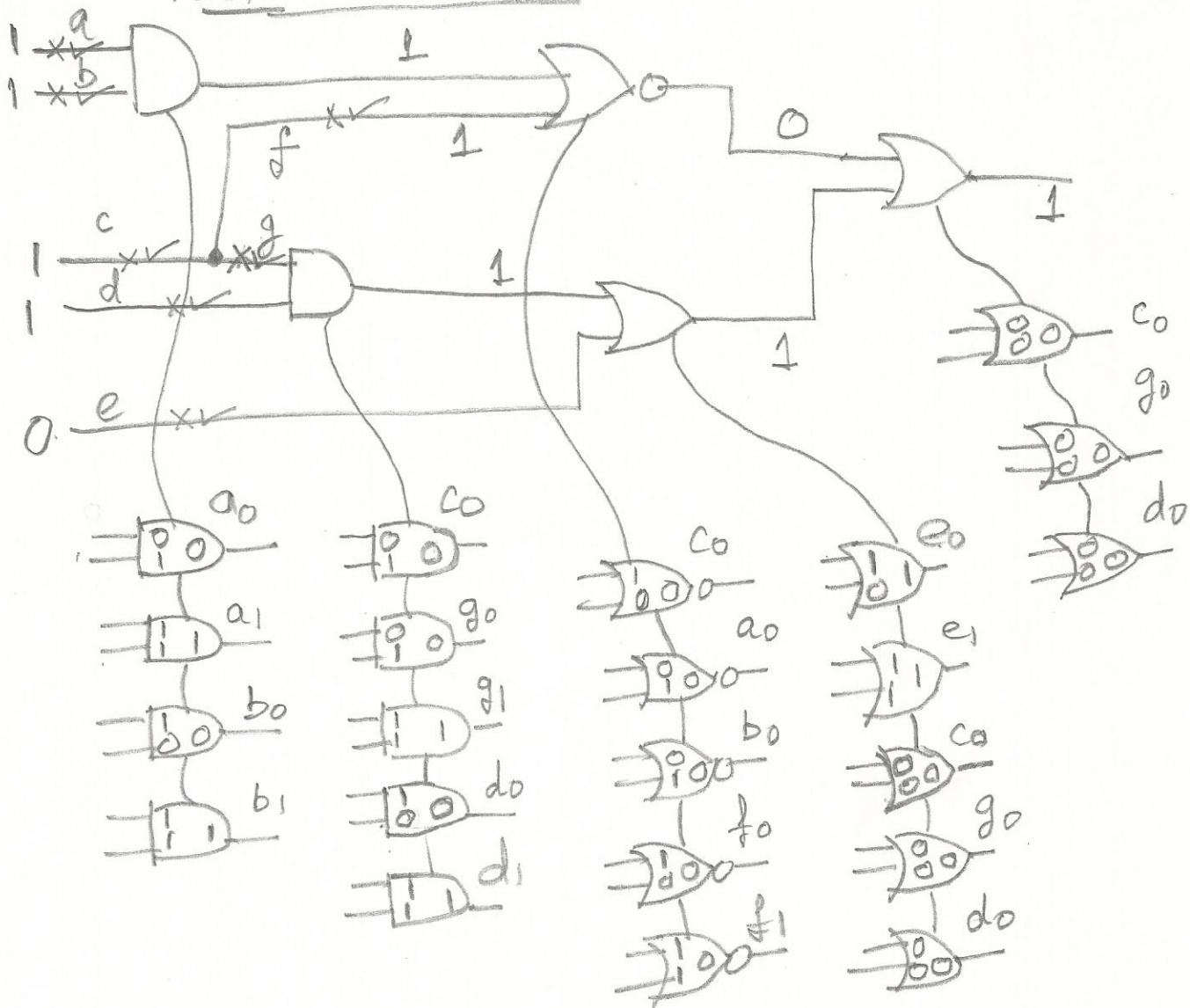

Detected: Co, go, do .

PROBLEM 3 TEST 1.

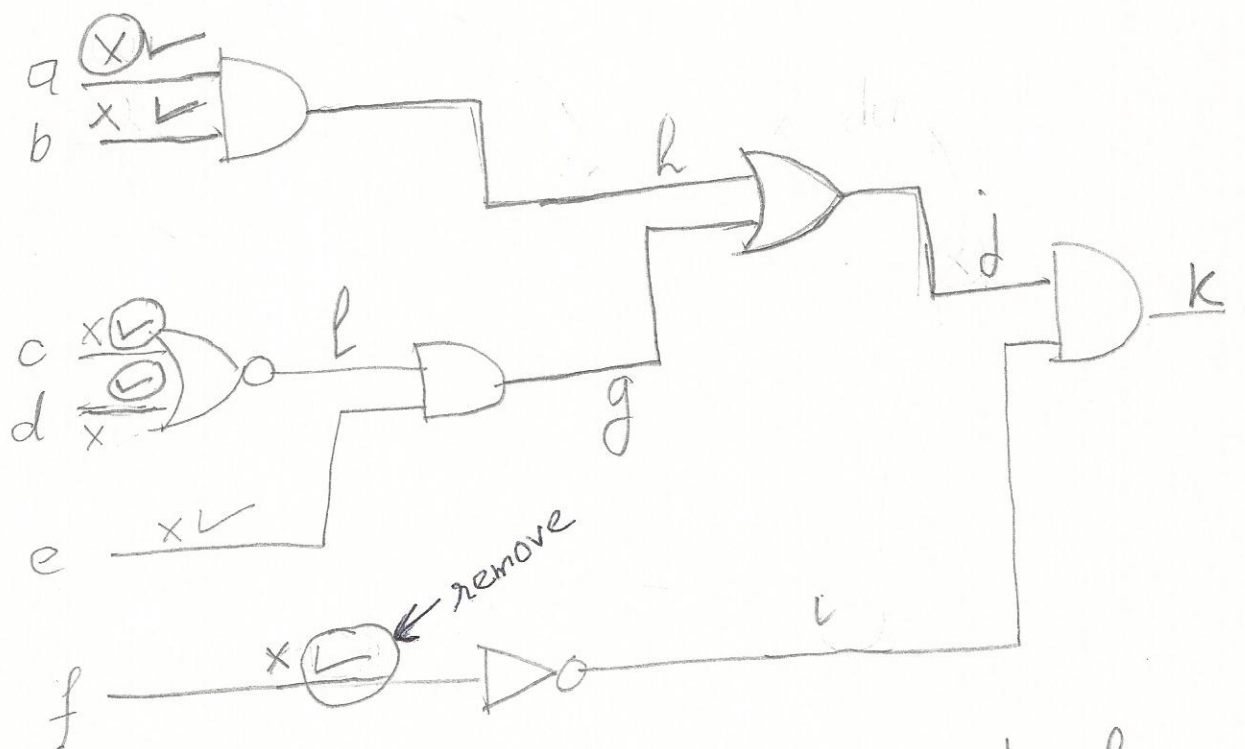

$$1. \left. \begin{array}{l} f_1 = l_0 = j_0 \\ h_0 = a_0 = b_0 \end{array} \right\} \text{ but } j_0 \text{ dominates } h_0 \text{ so remove } j_0$$

Removing $j_0 \Leftrightarrow$ removing f_1 .

$h_0 = b_0$ keep b_0 , remove a_0 .

$$2. c_1 = d_1 = l_0 = e_0. \text{ So remove } c_1 \text{ and } d_1.$$

So list of faults =

$$= \{a_1, b_1, b_0, c_0, d_0, e_0, e_1, f_0\}$$


PROBLEM 4 TEST 1.

$$e = w + \bar{w}x = w + x$$

$$d = e + \bar{e}y = e + y$$

$\{b_0, g_0\}$ or $\{b_0, h_1\}$ are undetectable

PROOF:

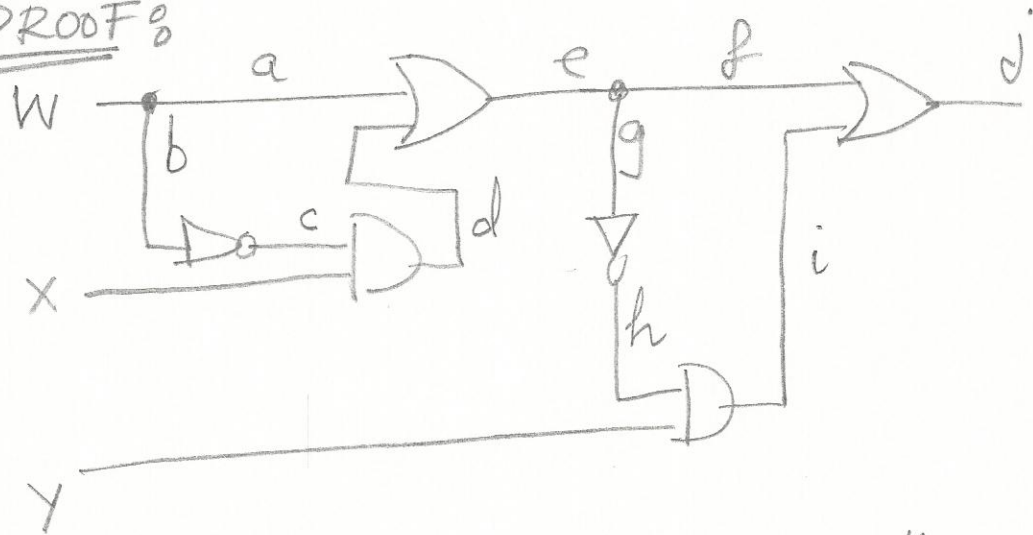

Hint: $e = w + x$ is obtained by setting $c = 1$. $\Leftrightarrow c_1$ is undetectable

but $c_1 = b_0$, so b_0 is undetectable.

Similarly $d = e + y$ is obtained by setting $h = 1$.

$\Rightarrow h_1$ is undetectable $\Rightarrow g_0$ is undetectable