

Q.4.5 (b) Typo - Test = {0011}

Correction – Test = {0111}

Q.4.8 (b) $Z_{1a0} = C'$ and $Z_{1c0} = C'$

$$Z_{2a0} = ABC \text{ and } Z_{2c0} = AB$$

$$Z_{1ff} = C' + AB \text{ and } Z_{2ff} = AB + ABC = AB \cdot (1 + C) = AB$$

$$\text{Test to distinguish a s-a-0} \Rightarrow Z_{1ff} \text{ XOR } Z_{1a0} = 1$$

$$\Rightarrow C' = 0 \text{ and } AB = 1$$

$$\Rightarrow ABC = 111$$

$$\Rightarrow Z_{2ff} \text{ XOR } Z_{2a0} = 1$$

$$\Rightarrow ABC \text{ XOR } AB = 1$$

$$\Rightarrow ABC = 110$$

$$\text{Test to distinguish c s-a-0} \Rightarrow Z_{1ff} \text{ XOR } Z_{1c0} = 1$$

$$\Rightarrow C' = 0 \text{ and } AB = 1$$

$$\Rightarrow ABC = 111$$

$$\Rightarrow Z_{2ff} \text{ XOR } Z_{2c0} = 1$$

$$\Rightarrow AB \text{ XOR } AB = 0$$

$$\text{Test for a s-a-0} \Rightarrow \{11X\}$$

$$\text{Test for c s-a-0} \Rightarrow \{111\}$$

Since tests exist for both the faults, both the faults are detectable.

For the faults to be distinguishable, there must exist a test vector which not only detects the faults(i.e gives output values different from fault free values) but also gives different outputs for each fault.

$$1. Z_{1ff} \text{ XOR } Z_{1a0} = 1$$

$$2. Z_{2ff} \text{ XOR } Z_{2a0} = 1$$

$$3. Z_{1ff} \text{ XOR } Z_{1c0} = 1$$

$$4. Z_{2ff} \text{ XOR } Z_{2c0} = 1$$

$$5. Z_{1a0(111)} \text{ XOR } Z_{1c0(111)} = 1$$

$$6. Z_{2a0(111)} \text{ XOR } Z_{2c0(111)} = 1$$

Since 111 is the common test vector, on evaluating the above equations with it, it is seen that 111 does not satisfy 5 and 6.

Therefore, the two faults are detectable but indistinguishable.